

Total No. of Questions : 8]

SEAT No. :

PB4531

[6261]-44

[Total No. of Pages :3

S.E.(Computer Engineering)
DIGITAL ELECTRONICS AND LOGIC DESIGN
(2019 Pattern) (Semester - III) (210245)

Time : 2½ Hours]

[Max. Marks :70

Instructions to the candidates:

- 1) *Answers Q.1 or Q.2, Q.3 or Q.4, Q.5 or Q.6, Q.7 or Q.8.*
- 2) *Neat diagrams must be draw wherever necessary.*
- 3) *Assume Suitable data if necessary.*

- Q1)** a) What are the applications of Flip-Flop? Explain shift register. [6]
- b) Design a sequence generator to generate the sequence. [6]
.....1, 3, 5, 7, 1.....
- c) Desgin the 2-bit synchronous UP counter using T - F/F. [6]

OR

- Q2)** a) Explain S-R Flip-Flop and J-K Flip Flop using NOR gate. [6]
- b) Convert the following Flip Flops [6]
i) D to T
ii) Jk to D
- c) Draw and explain 4 bit Ripple down Counter. [6]

- Q3)** a) Implement the following Boolem function using PAL. [6]
 $F1 = \sum m(0,3,5,7,9,10,11,14,15)$
 $F2 = \sum m(2,3,12,14)$
- b) Draw block diagram of PLA device and explain in detail. [6]
- c) What is ASM chart? Design ASM chart for 3-Bit gray code sequence with up-down conditions. [5]

OR

P.T.O.

- Q4)** a) Implement gray to binary code using PLA. [6]
- b) Implement the following Boolean functions using PAL [6]
 $X1(A, B, C, D) = \sum m(0, 2, 6, 7, 8, 9, 12, 13)$
 $X2(A, B, C, D) = \sum m(3, 6, 7, 11, 14, 15)$
- c) What is ASM Chart? State & Explain basic components of ASM chart. Also explain the salient features of ASM chart [5]

- Q5)** a) Draw and explain the operation of TTL NAND gate using 2-bit input. [6]
- b) Explain with a neat diagram CMOS NAND gate. [6]
- c) Define the following terms and mention its standard value for TTL logic family. [6]
- Noise immunity
 - Power Dissipation
 - Figure of Merit

OR

- Q6)** a) Draw and explain CMOS inverter. [6]
- b) Explain TTL open collector. [6]
- c) Compare CMOS and TTL logic family. [6]

- Q7)** a) For memory operations draw digital circuits using ALU and shift registers. [6]
- b) What is Microprocessor? List different applications of Microprocessor. [6]
- c) What are the different types of buses used in Microprocessor? [5]

OR

- Q8) a)** Explain in brief basic arithmetic operations using ALU IC 74181. [6]
- b) Write a short note on [6]
- i) Address Bus
 - ii) Data Bus
 - iii) Control Bus
- c) Write a short note on Memory organization of Microprocessor. [5]
