

Total No. of Questions : 8]

SEAT No. :

PA-1205

[Total No. of Pages : 2

[5925] 227

S.E. (Electrical)

**ANALOG AND DIGITAL CIRCUITS ELECTRONICS**

(2019 Pattern) (Semester-III) (203143)

Time : 2½ Hours]

[Max. Marks : 70

Instructions to the candidates:

- 1) Solve Q.1 or Q.2, Q.3 or Q.4, Q.5 or Q.6, Q.7 or Q.8.
- 2) Neat diagrams must be drawn wherever necessary.
- 3) Figures to the right indicate full marks.
- 4) Use of Calculator is allowed.
- 5) Assume Suitable data is necessary.

Q1) a) Write a short note on FPGA. [6]

b) What is DRAM? What are its advantages and disadvantages? [6]

c) Describe in detail Read Only Memory (ROM). [6]

OR

Q2) a) What is semiconductor memory? Enlist advantages of it. [6]

b) Write a short note on sequential memories. [6]

c) Write a short note on CPLD. [6]

Q3) a) Explain with neat diagram and output waveforms, Op-Amp as a zero crossing detector? [5]

b) Draw circuit of Op-Amp as V-I converter. Also explain its working. [5]

c) Explain generation of saw tooth waveform using OP-AMP. Draw input & output waveforms. [8]

OR

Q4) a) Draw neat diagram of Op Amp as a Schmitt trigger and explain its working. [5]

b) With neat pin diagram explain function of each pin of IC 741 [5]

c) Explain generation of sine waveform using OPAMP. Draw input & output wave forms [8]

P.T.O.

- Q5)** a) Explain the function of LM 317 as adjustable voltage regulator. [5]  
b) With neat diagram explain working of IC 555 as a Astable Multivibrator.[5]  
c) Explain High pass filter using op-amp with its frequency response. [7]

OR

- Q6)** a) What is voltage regulator? Write any two applications of voltage regulator. [5]  
b) Explain Low pass filter using op-amp with its frequency response. [7]  
c) With neat diagram explain working of IC 555 as a Monostable Multivibrator. [5]

- Q7)** a) Explain working of single phase half wave rectifier with RL load. [5]  
b) Explain the working o single-phase full wave centre tapped rectifier with pure resistive laod. [7]  
c) Define following terms [5]  
i) form factor  
ii) Ripple factor  
iii) TUF

OR

- Q8)** a) With the help of circuit diagram and relevant waveforms, explain the operation of a 3-phase bridge rectifier with resistive load. [7]  
b) Compare single phase HWR and single phase FWR. [5]  
c) Draw neat diagram and explin single phase half wave rectifier with pure resistive laod. [5]

