

Total No. of Questions : 4]

SEAT No. :

PA-11

[Total No. of Pages : 2

[5931]-17

S.E. (Electrical)

ANALOG & DIGITAL ELECTRONICS
(2019 Pattern) (Semester - I) (203143)

Time : 1 Hour]

[Max. Marks : 30

Instructions to the candidates:

- 1) Solve Q1 or Q2, Q3 or Q4.
- 2) Figures to the right indicate full marks.
- 3) Neat diagrams must be drawn wherever necessary.
- 4) Assume suitable data, if necessary.

Q1) a) Plot the following Boolean expressions on K Map [5]

i) $Y = ABC + \overline{A}BC + AB\overline{C}$

ii) $Y = \overline{A}BCD + A\overline{B}CD + AB\overline{C}D + ABC\overline{D} + ABCD$

b) Minimize the following Boolean function-using K Map [5]

$F(A, B, C, D) = \sum m(0, 1, 3, 5, 7, 8, 9, 11, 13, 15)$

c) Describe the function of half adder with its logic diagram and truth table. [5]

OR

Q2) a) Draw logical diagram of 8:3 encoder. Explain its working with truth table. [5]

b) Prove the following using the Boolean algebra theorems [5]

i) $A + \overline{A}.B + A.\overline{B} = A + B$

ii) $A.B + \overline{A}.B + \overline{A}.\overline{B} = \overline{A} + B$

c) What is meant by SOP and POS form of reduction? Explain one with example. [5]

P.T.O.

- Q3)** a) State difference between synchronous and asynchronous counters (5 points). [5]
- b) Draw and explain Asynchronous Up-Down counter. [5]
- c) What is meant by shift register? List different types of shift register. [5]

OR

- Q4)** a) Design and explain the operation of MOD 10 asynchronous counter. [5]
- b) Explain twisted ring counter in detail with truth table. [5]
- c) Draw circuit diagram and explain 4 bit universal shift register. [5]

□□□