

Total No. of Questions : 8]

SEAT No. :

PB-3614

[Total No. of Pages : 3

[6261]-19

S.E. (Electrical)

ELECTRICAL MEASUREMENTS & INSTRUMENTATION

(2019 Pattern) (Semester - III) (203144)

Time : 2½ Hours]

[Max. Marks : 70

Instructions to the candidates:

- 1) Answer Q1 or Q2, Q3 or Q4, Q5 or Q6, Q7 or Q8.
- 2) Neat diagrams must be drawn wherever necessary.
- 3) Figures to the right side indicate full marks.
- 4) Assume suitable data if necessary.

Q1) a) With neat circuit diagram and necessary phasor diagram, prove that in two wattmeter method for measurement of 3 phase power in balanced R-L load, total power, $W_1 + W_2 = \sqrt{3} V_L I_L \cos \phi$. [8]

b) A circuit takes 10 A at 200 V. The power absorbed is 1000 W. If resistance of current coil is 0.15Ω and that of pressure coil is 5000Ω , calculate the error when [6]

- i) Pressure coil is connected on supply side of the circuit
 - ii) Pressure coil is connected on load side of the circuit
- c) Write a note on low power factor wattmeter. [4]

OR

Q2) a) When the power of 3 phase balanced star connected load is measured by single wattmeter method with current coil in R phase and pressure coil between R phase and neutral, it showed 6 kW. The load current is 30 A at 400 V. What will be the reading of wattmeter if connections of current coil remain same but pressure coil is connected between Y and B phases. [5]

b) With neat diagram, derive the torque equation of a single phase electro-dynamometer type wattmeter. [7]

c) Explain error due to inductance of pressure coil in single phase wattmeter. Hence state significance of multiplying factor. [6]

P.T.O.

- Q3)** a) In a test of 30 min duration with a constant current of 12 A through UPF load, meter registered 1.50 kWh. If the meter is subsequently used on 230 V supply, determine its error and state whether meter is running fast or slow. [5]
- b) Explain with neat diagram and necessary phasor diagrams, how single-phase energy meter can be calibrated at different power factors using resistive load. [7]
- c) Write a note on TOD meter [5]

OR

- Q4)** a) A single phase energy meter is supplying power to a unity p.f load at 240 V, 4.4 A for a period of 5 hours. [7]
- i) If disc makes 2400 revolutions, calculate the meter constant
- ii) Calculate the p.f. of the load if the load is operated for 4 hours at 240 V, 5 A and meter making 1500 revolutions.
- b) Draw neat diagram of induction type energy meter, label all the parts and explain its construction and working. [10]

- Q5)** a) With neat diagram, explain Pirani gauge for measurement of low pressure [6]
- b) Draw the representation of lissajous patterns for following frequency ratios [4]
- i) 2:1 ii) 1:3 iii) 1:1 iv) 2:3
- c) Give detailed classification of transducers along with examples of each type. [8]

OR

- Q6)** a) Explain construction and working of cathode ray oscilloscope. [7]
- b) Explain resistive pressure transducers. [5]
- c) Define pressure? Explain importance of pressure measurement in electrical systems hence give min five units in which pressure can be measured. [6]

- Q7) a)** With neat diagram, explain capacitive method for level measurement. [6]
- b) Explain construction and working of bonded and unbonded strain gauge. [6]
- c) Draw and justify characteristic of LVDT hence give various specifications of LVDT. [5]

OR

- Q8) a)** Explain with neat diagram, construction and working of foil strain gauge [6]
- b) Explain how level can be measured using hydraulic method. [7]
- c) Define strain, state importance of displacement measurement in electrical system. [4]

