

Total No. of Questions : 8]

SEAT No. :

PC2794

[6352]-18

[Total No. of Pages : 2

S.E. (Electrical Engineering)

ANALOG AND DIGITAL ELECTRONICS

(2019 Pattern) (Semester-III) (203143)

Time : 2½ Hours]

[Max. Marks : 70

Instructions to the candidates:

- 1) Solve Q.1 or Q.2, Q.3 or Q.4, Q.5 or Q.6, Q.7 or Q.8.
- 2) Figures to the right indicate full marks.
- 3) Neat diagrams must be drawn wherever necessary.
- 4) Assume suitable additional data, if necessary.
- 5) Use of non-pro programmable calculator is allowed.

Q1) a) Explain CPLD. [6]

b) Compare Between SRAM & DRAM. [6]

c) What is semiconductor memory? Enlist advantages of it. [6]

OR

Q2) a) Compare ROM & PROM [6]

b) Write a short note on EPROM. [6]

c) Explain PAL. [6]

Q3) a) With neat pin diagram explain function of each pin of IC 741 [5]

b) Explain with Neat diagram of peak detector. [6]

c) Explain generation of Triangular waveform using Op-Amp. Draw input & output waveforms. [7]

OR

Q4) a) Explain with neat diagram and output waveforms, Op-Amp as a Comparator. [5]

b) Explain Instrumentation amplifier with Circuit Diagram. [6]

c) Explain generation of Square waveform using Op-Amp. Draw input & output waveforms [7]

P.T.O.

- Q5)** a) With neat diagram explain working of IC 555 as a Mono stable Multivibrator. [5]
b) Explain Sequence generator. [5]
c) Explain High pass filter using op-amp with its frequency response. [7]

OR

- Q6)** a) Explain the function of IC 78xx as adjustable voltage regulator. [5]
b) What is voltage regulator? Write any two applications of voltage regulator. [5]
c) With neat diagram explain working of IC 555 as a Astable Multivibrator. [7]

- Q7)** a) Explain working of single phase half wave rectifier with R load. [5]
b) Compare single phase & three phase rectifier. [5]
c) With the help of circuit diagram and relevant waveforms, explain the operation of a 3-phase bridge rectifier with resistive load. [7]

OR

- Q8)** a) Define [4]
i) Form factor
ii) TUF
b) Explain working of single phase half wave rectifier with RL load. [6]
c) Explain the working of single-phase full wave centre tapped rectifier with pure resistive load. [7]

