

Total No. of Questions : 8]

SEAT No. :

PD-4054

[Total No. of Pages : 2

[6402]-13

S.E. (Electrical)

203143: Analog and Digital Electronics
(2019 Pattern) (Semester - III)

Time : 2½ Hours]

[Max. Marks : 70

Instructions to the candidate:

- 1) Solve Q1 or Q2, Q3 or Q4, Q5 or Q6, Q7 or Q8.
- 2) Neat diagrams must be drawn wherever necessary.
- 3) Figures to the right side indicate full marks.

Q1) a) Explain working of SRAM with diagram. [6]

b) Explain Programmable Logic Array. Implement the following Boolean functions using PLA: [6]

$$A = XY + XZ'$$

$$B = XY' + YZ + XZ'$$

c) Write a short note on FPGA [6]

OR

Q2) a) Explain working of DRAM with diagram. [6]

b) Write a short note on CPLD. [6]

c) Explain Programmable Array Logic in detail. [6]

Q3) a) Explain OPAMP as voltage to current converter. [5]

b) Explain working of OPAMP as instrumentation amplifier. [5]

c) Explain the working of OPAMP as a comparator along with circuit diagram and input and output waveforms. [8]

OR

P.T.O.

- Q4)** a) With the help of neat diagrams, explain OPAMP as peak detector. [5]
b) Define the characteristics of practical OPAMP. [5]
c) Explain generation of saw tooth waveform using OPAMP. Draw input & output waveforms. [8]

- Q5)** a) Explain High pass filter using op-amp with its frequency response. [5]
b) Explain the function of LM 317 as adjustable voltage regulator. [5]
c) Draw the diagram of IC 555 configured in monostable mode. Draw necessary waveforms. [7]

OR

- Q6)** a) What is the difference between fixed and variable voltage regulators? Explain IC78XX and IC 79XX series regulators. [5]
b) Explain the operation of IC555 as astable multivibrator along with waveforms. [5]
c) Draw and explain frequency response characteristic of ideal and practical Low Pass Filter. [7]
- Q7)** a) Explain working of single phase full wave bridge rectifier supplying R-L load. [5]
b) Draw neat diagram and explain single phase half wave rectifier with pure resistive load. Also define peak inverse voltage. [5]
c) Explain in detail the working of center tapped rectifier connected to the R-L load. [7]

OR

- Q8)** a) Explain working of single phase half wave rectifier with RL load. [5]
b) Explain the working of single-phase full wave centre tapped rectifier with pure resistive load. Also draw the input and output waveforms. [5]
c) With the help of circuit diagram and relevant waveforms, explain the operation of a 3-phase bridge rectifier with resistive load. [7]

