

Total No. of Questions : 8]

SEAT No. :

PE4247

[Total No. of Pages : 2

[6582]-18

S.E. (Electrical Engineering)

ANALOG AND DIGITAL ELECTRONICS

(2019 Pattern) (Semester - III) (203143)

Time : 2½ Hours]

[Max. Marks : 70

Instructions to the candidates:

- 1) *Solve Q1 or Q2, Q3 or Q4, Q5 or Q6, Q7 or Q8.*
- 2) *Figures to the right indicate full marks.*
- 3) *Neat diagrams must be drawn wherever necessary.*
- 4) *Assume suitable additional data, if necessary.*
- 5) *Use of non-programmable calculator is allowed.*

- Q1)** a) Write a comparison between CPLD and FPGA. [4]
b) Draw a circuit of basic static MOS RAM cell. Explain how information is stored in it. [6]
c) State two advantages of PLD over fixed function IC and application specific IC. What is the difference between PLA, PAL and PROM. [8]

OR

- Q2)** a) What do you mean by configurable device. [4]
b) What is FPGA? Explain its basic structure. [6]
c) Design a 3-bit Gray to Binary code converter. Implement it using suitable PROM. Draw the PROM table and logic Diagram. [8]

- Q3)** a) What is the role of OP-AMP as an instrumentation amplifier? [3]
b) Explain how OP-AMP work as a closed loop inverting amplifier, Draw neat waveforms. Also derive gain of OP-AMP for the same. [6]
c) Explain with neat diagram Schmitt trigger as an application of OP-AMP. [8]

OR

- Q4)** a) Write classification of open loop configuration of OP-AMP? Explain any one form it. [3]
b) Draw neat diagram. Explain OP-AMP as a Peak detector. [6]
c) Explain voltage and current converter for grounded type load. [8]

P.T.O.

- Q5) a)** Explain the function of 78XX. [4]
- b) Draw and explain IC 555 as an Astable multivibrator with neat connection diagram. [6]
- c) Explain how triangular waveform can be generated using OP-AMP? Also draw waveform. [8]

OR

- Q6) a)** Draw the diagram and waveform of IC 555 as monostable multivibrator. [4]
- b) Explain the operation of low pass filter with a neat circuit diagram. [6]
- c) Explain the function of LM 317 as a voltage regulator. [8]

- Q7) a)** Define for half wave rectifier : [3]
- i) Efficiency
- ii) Form factor
- iii) Ripple factor
- b) Explain the working of single phase half wave rectifier with RL load with neat sketch and draw its waveform. [6]
- c) Draw and explain three-phase bridge rectifier with R-Load. Also draw input voltage and output voltage waveform. [8]

OR

- Q8) a)** Define for Full wave rectifier : - [3]
- i) Average output voltage
- ii) RMS output voltage
- iii) Peak inverse voltage
- b) Compare single phase half-wave and full - wave rectifier. [6]
- c) Draw and explain three-phase half wave rectifier with R load with adequate wave form. [8]

x

x

x