

Total No. of Questions : 4]

SEAT No. :

PE-535

[Total No. of Pages : 2

[6578]-8

S.E. (Electrical) (Insem.)

ANALOG AND DIGITAL ELECTRONICS

(2019 Pattern) (Semester - III) (203143)

Time : 1 Hour]

[Max. Marks : 30

Instructions to the candidates:

- 1) Answer Q.1 or Q.2, Q.3 or Q.4.
- 2) Figures to the right indicate full marks.
- 3) Neat diagram must be drawn wherever necessary.
- 4) Make suitable assumptions, if necessary.

Q1) a) State De-Morgan's Theorem and using Boolean algebra prove the following. [5]

$$AB + CD = \overline{\overline{AB} \cdot \overline{CD}}$$

- b) With a neat Block diagram explain function of an Encoder and Decoder. Give its applications. [5]
- c) Minimize the logic function in POS form by using K-map [5]

$$f(A, B, C, D) = \Pi M(4, 6, 10, 12, 13, 15)$$

OR

- Q2) a) Explain SOP and POS Form for Four Variable. [5]
- b) Draw and explain full adder. [5]
  - c) Design a hazard free circuit in AND-OR Configuration for the logic function. [5]

$$Y(A, B, C, D) = \Sigma m(1, 3, 5, 7, 12, 13)$$

- Q3) a) What is the difference between combinational circuit and Sequential circuit. [5]
- b) Define Synchronous and Asynchronous Counter and Explain 3-Bit Synchronous UP Counter. [5]
  - c) Explain the operation of 4-Bit Serial in Serial out shift register. [5]

P.T.O.

OR

- Q4)** a) Explain Different type of Shift Register with Applications. [5]  
b) Design a synchronous MOD-6 Counter using T flip-flop. [5]  
c) Draw and Explain Ring Counter. [5]

\*\*\*