

Total No. of Questions : 4]

SEAT No. :

PE-536

[Total No. of Pages : 2

[6578]-9

**S.E. (Electrical Engineering) (Insem.)
ELECTRICAL MEASUREMENTS AND
INSTRUMENTATION
(2019 Pattern) (Semester - III) (203144)**

Time : 1 Hour]

[Max. Marks : 30

Instructions to the candidates:

- 1) *Solve Q.1 or Q.2, Q.3 or Q.4.*
- 2) *Figures to the right side indicate full marks.*
- 3) *Assume suitable data if necessary.*

Q1) a) Explain the following terms related to instrument transformer: [8]

- i) Transformation ratio
- ii) Nominal ratio
- iii) Turns ratio
- iv) Burden

b) Draw a neat schematic diagram of attraction type moving iron instrument and explain deflecting, controlling, and damping system used in it. [7]

OR

Q2) a) With a suitable diagram explain construction and working of PMMC instrument. [8]

b) Explain in brief static and dynamic characteristics of instrument. [7]

Q3) a) With a circuit diagram derive the equation for balance in the case of Maxwell's inductance bridge. Draw the phasor diagram for balance condition. [7]

b) With neat diagram, derive the expression for unknown resistance in Wheatstone bridge. [8]

OR

P.T.O.

Q4) a) With suitable circuit diagram explain ammeter and voltmeter method for measurement of resistance. State two disadvantages of this method. [7]

b) Maxwell's inductance capacitance bridge is used to measure an unknown inductance in comparison with capacitance the various values are

$R_2 = 400\Omega$, $R_3 = 600\Omega$, $R_4 = 1000\Omega$, $C_4 = 0.5\mu\text{F}$ Calculate values of R_1 & L_1 . Also calculate Q factor of coil if frequency is 1000Hz. [8]
