

[5869]-238

S.E. (Electrical Engineering)

NETWORK ANALYSIS

(2019 Pattern) (Semester - IV)

Time : 2½ Hours]

[Max. Marks : 70

Instructions to the candidates:

- 1) Answer Q.1 or Q.2, Q.3 or Q.4, Q.5 or Q.6, Q.7 or Q.8.
- 2) Neat diagrams must be drawn wherever necessary.
- 3) Figures to the right indicate full marks.
- 4) Use of calculator is allowed.
- 5) Assume suitable data, if necessary.

- Q1) a) In the circuit shown in fig. no. 1 initially switch is kept open for long time. At $t = 0$, switch K is closed. Obtain expression for current at $t > 0$. Find the value of the current at $t = 0.25$ sec. What will be the current in circuit in one time constant period. [7]

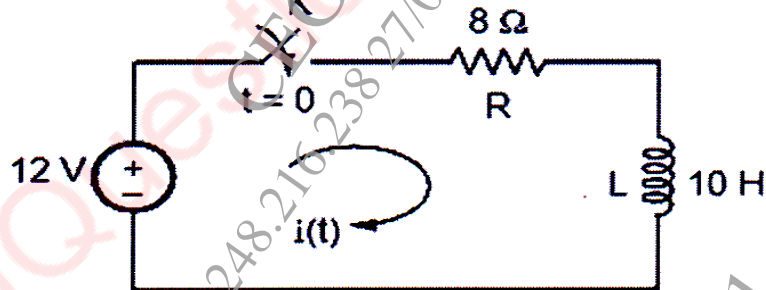


Fig. No. 1

- b) Explain the behaviour of R, L and C elements for transients. Mention the representation at the instant of switching. [5]
- c) Obtain the expression for voltage across capacitor in series RC circuit connected to a. d. c. voltage V for $t > 0$. Assume initial charge across capacitor is zero. [5]

OR

P.T.O.

Q2) a) What is time constant? Explain time constant in case of series R-L and series R-C circuit. [7]

b) A series R-L-C circuit shown in fig. no. 2 is excited by DC voltage source. Find current $i(t)$ using conventional method. The switch is closed at $t = 0$ [10]

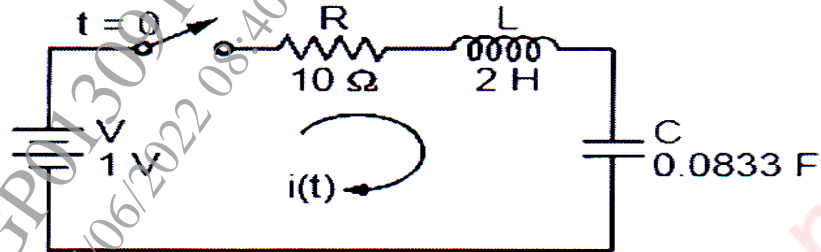


Fig. No. 2

Q3) a) State and prove initial and final value theorem. [6]

b) Find the Laplace transform of the function. [6]

$$f(t) = t \text{ for } 0 < t < 1$$

$$= 0 \text{ for } t > 1.$$

c) State any six properties of Laplace Transform. [6]

OR

Q4) a) Derive the relation between unit step function and unit ramp function. [6]

b) Find the Laplace transform of $\sin \omega t$. [6]

c) Find $i(t)$, by using convolution integral : [6]

$$F(s) = \frac{1}{s^2 + 9s + 18}$$

Q5) a) Express hybrid parameters in terms of transmission line parameters. [9]

b) Find Z parameters of the network shown in figure no. 3 [8]

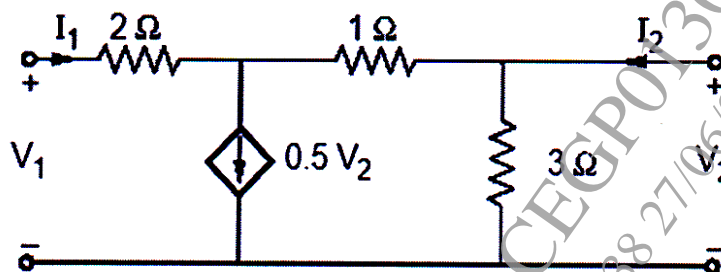


Fig. No. 3

OR

- Q6)** a) What is high pass filter? Derive the expression for the cut-off frequency of prototype low pass filter in terms of L and C. [9]
- b) Design a prototype high pass filter sections if design impedance $R_0 = 600$ ohm and cut-off frequency $f_c = 1000$ Hz. [8]

- Q7)** a) State and explain all possible network functions of one port network. [9]
- b) Determine the driving point impedance for the network shown in fig. No.4 [9]

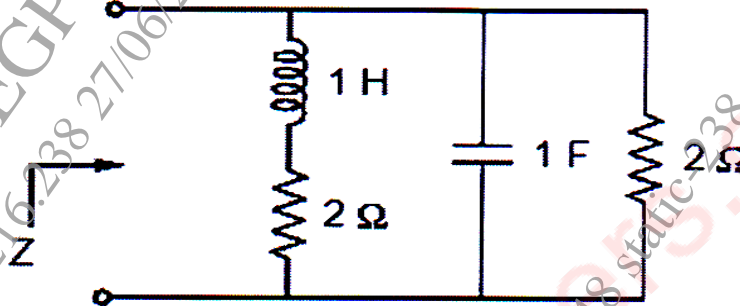


Fig. No. 4

OR

- Q8)** a) What is pole-zero plot? Explain with suitable example. [9]
- b) Obtain the pole zero plot in the s-plane of the driving point impedance function for the network shown in fig. no. 5 [9]

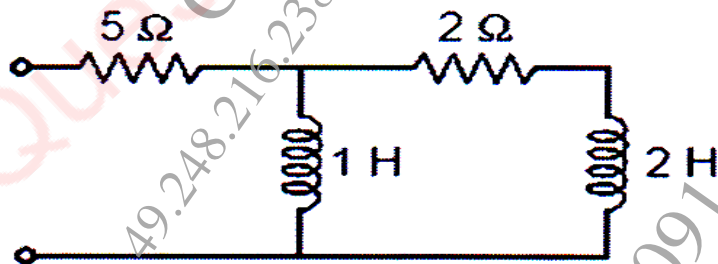


Fig. No. 5

