

Total No. of Questions : 4]

SEAT No. :

PA-10291

[Total No. of Pages : 2

[6008]-213

S.E. (Electrical Engineering) (In-Sem.)

ELECTRICAL MACHINES - I

(2019 Pattern) (Semester - II) (203146)

Time : 1 Hour]

[Max. Marks : 30

Instructions to the candidates:

- 1) Solve Q1 or Q2, Q3 or Q4.
- 2) Figures to the right indicate full marks.
- 3) Neat diagrams must be drawn wherever necessary.
- 4) Assume suitable data, if necessary.
- 5) Use of non-programmable calculator is allowed.

Q1) a) Write mathematical expression for the losses in case of transformer. State the condition for maximum efficiency of transformer. [3]

b) A 10 kVA single-phase transformer, rated for 2000/400 Volt has resistances and leakage reactances as follows. [6]

Primary winding : $R_1 = 5.5 \text{ Ohm}$, $X_1 = 12 \text{ Ohm}$.

Secondary winding : $R_2 = 0.2 \text{ Ohm}$, $X_2 = 0.45 \text{ Ohm}$.

Determine the full load voltage regulation 0.8 power-factor lagging

c) Give any 3 points of comparison between autotransformer and normal transformer. [6]

OR

Q2) a) State the expression of voltage regulation of transformer in terms of all voltage drops. State any two factors affecting voltage regulation of transformer. [3]

b) A 100-kVA distribution transformer supplying light and fan loads has full-load copper-loss 1.5 kW and core-loss 2 kW. During 24 h in a day the transformer is loaded as follows : [6]

6 AM to 10 AM (4 hrs) Half-load

10 AM to 6 PM (8 hrs) One-fourth load

6 PM to 10 PM (4 hrs) Full-load

10 PM to 6 AM (8 h) Negligible load

Calculate the all-day efficiency of the transformer.

c) Draw phasor diagram of transformer for leading power factor condition. Mark all parameters in the phasor diagram. [6]

P.T.O.

- Q3)** a) State one application of each for following connections of transformer -
i) Y-Y Connection ii) Y - Delta connection iii) Delta –Y Connection. [3]
- b) With suitable circuit diagram and phasor diagram explain Scott connection of transformer. [6]
- c) State the necessity of polarity test for transformer. Draw circuit diagram of polarity test on single phase transformer. [6]

OR

- Q4)** a) State any three advantages of V-V Connection. [3]
- b) Two 1-Phase transformers have equal turns. Their impedances are $(0.5+j3)$ Ohm and $(0.6+j10)$ Ohm with respect to the secondary. If they operate in parallel, determine how they will share a total load of 100 kW at p.f. 0.8 lagging? [6]
- c) Explain parallel operation of two 1 phase transformers for following condition-Same kVA rating and unequal impedance. [6]