

S.E. (Electrical Engineering)

NETWORK ANALYSIS

(2019 Pattern) (Semester - IV) (203147)

Time : 2 1/2 Hours]

[Max. Marks : 70

Instructions to the candidates:

- 1) Solve Q1 or Q2, Q3 or Q4, Q5 or Q6, Q7 or Q8.
- 2) Figures to the right indicate full marks.
- 3) Neat diagrams must be drawn wherever necessary.
- 4) Assume suitable additional data, if necessary.
- 5) Use of non-programmable calculator is allowed.

Q1) a) Derive the expressions for voltage across resistance and voltage across inductor in series RL circuit connected to a d.c. voltage V for $t > 0$. Assume that initial current through inductor is zero. [5]

b) In the network shown in Fig. 1, switch is closed at $t = 0$. Before closing the switch capacitor was in uncharged state. Find the values of

$$i(0^+), \frac{di(0^+)}{dt}, \frac{d^2i(0^+)}{dt^2} \quad [6]$$

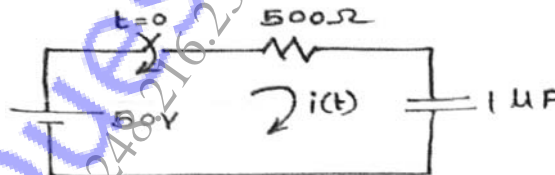


Fig. 1

c) For the network shown in Fig. 2, steady state is reached with switch closed. The switch is opened at $t = 0$. Obtain expressions for $i_L(t)$ for $t > 0$. [6]

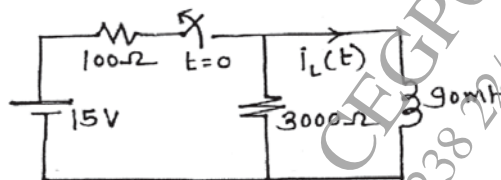


Fig. 2

OR

P.T.O.

Q2) a) Derive the expressions for voltage across resistance and voltage across capacitor in series RC circuit connected to a d.c. voltage V for $t > 0$. Assume that initial voltage across capacitor is zero. [5]

b) In the network shown in Fig. 3. switch is closed at $t=0$. Assume initial current of inductor to be zero. Find the values of [6]

$$i(0^+), \frac{di(0^+)}{dt}, \frac{d^2i(0^+)}{dt^2}$$

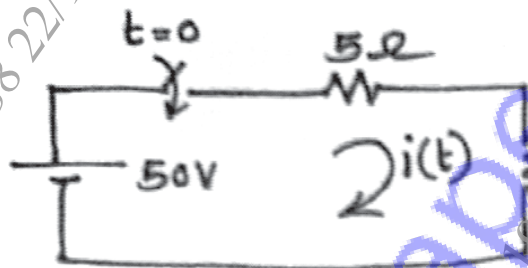


Fig. 3

c) The switch in the circuit shown in Fig. 4 is moved from position 1 to 2 at $t = 0$. Find expression for $V_c(t)$ for $t > 0$. [6]

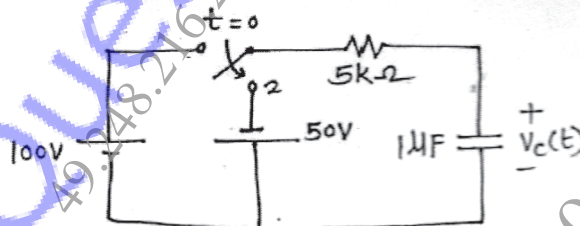


Fig. 4

Q3) a) Express following functions mathematically along with waveforms: [6]

- i) Step function. Unit Step function. Delayed Unit Step function
- ii) Ramp function. Unit Ramp function. Delayed Unit Ramp function

- b) In the network shown in Fig. 5, switch is moved from position a to b at $t=0$. Just before this switching the initial conditions were $i(0^-) = 2\text{ A}$ and $V_c(0^-) = 2\text{ V}$. Find the expression for current $i(t)$ using Laplace Transform method. Assume $R = 3\ \Omega, L = 1\text{ H}, C = 0.5\ \mu\text{F}, V_1 = 5\text{ V}$. [6]

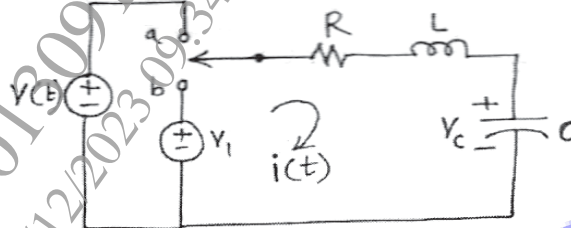


Fig. 5

- c) In the network shown in Fig. 6, switch is moved from position 1 to 2 at $t=0$. Find $i(t), \frac{di(t)}{dt}, \frac{d^2i(t)}{dt^2}$ at $t = 0^+$ by Laplace Transform approach.

[6]

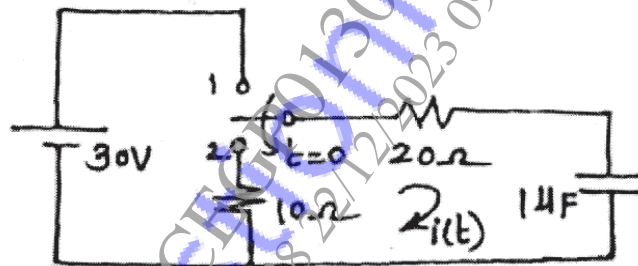


Fig. 6

OR

- Q4) a) State any six properties of Laplace Transform. [6]
 b) In the network shown in Fig. 7, the switch is moved from position a to b at $t=0$. Determine expression for $i(t)$ using Laplace Transform approach. [6]

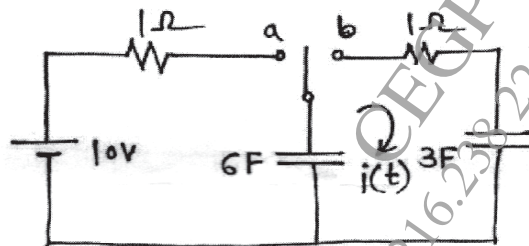


Fig. 7

- c) In the network shown in Fig. 8, switch is moved from position 1 to 2 at $t = 0$. Find expression for $i(t)$ by Laplace Transform approach. [6]

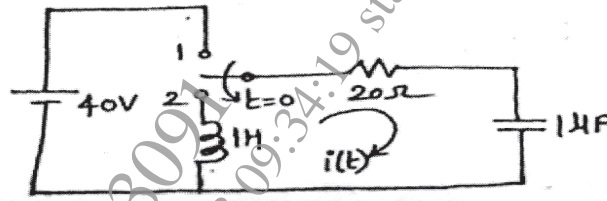


Fig. 8

- Q5) a) Design constant K low pass filter having cut-off frequency 1kHz and design impedance 400Ω in both the T and π configurations. [5]
 b) Find Z parameters of the network shown in Fig.9. [6]



Fig. 9

- c) Derive 'h' parameters in terms of 'Z' parameters for a two port network. [6]

OR

- Q6) a) Design constant k high pass filter having cut-off frequency 1000 Hz and design impedance 1000Ω in both the T and π configurations. [5]
 b) Find Y parameters of the network shown in Fig. 10. [6]

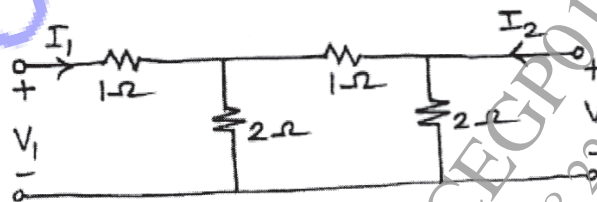


Fig. 10

- c) Derive 'Z' parameters in terms of 'Y' parameters for a two port network. [6]

- Q7) a) Define various network functions of a two port network. [6]
- b) Determine Driving Point Admittance function $Y_{11}(s)$ for the network in Fig. 11 and hence draw pole zero plot of $Y_{11}(s)$. [6]

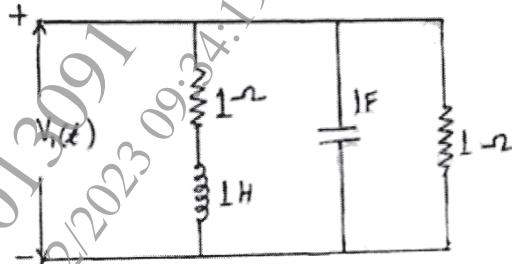


Fig. 11

- c) Plot Poles and Zeros for the network function $V(s) = \frac{s+20}{s(s+10)}$ and obtain time domain response. [6]

OR

- Q8) a) State restrictions on Poles and Zeros locations for transfer functions and driving point function. [6]
- b) Determine Driving Point Impedance function $Z_{11}(s)$ and Driving Point Admittance function $Y_{11}(s)$ for the network in Fig. 12. [6]

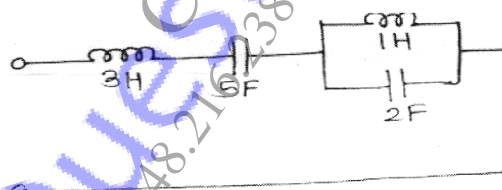


Fig. 12

- c) Plot Poles and Zeros for the network function $I(s) = \frac{10(s+2)}{s(s+5)}$ and obtain time domain response. [6]

