

Total No. of Questions : 8]

SEAT No. :

PE-4242

[Total No. of Pages : 3

[6582]-13

S.E. (Electrical Engineering)

NETWORK ANALYSIS

(2019 Pattern) (Semester - IV) (203147)

Time : 2½ Hours]

[Max. Marks : 70

Instructions to the candidates :

- 1) Answer Q1 or Q2, Q3 or Q4, Q5 or Q6, Q7 or Q8.
- 2) Neat diagrams must be drawn wherever necessary.
- 3) Figures to the right indicate full marks
- 4) Use of Calculator is allowed.
- 5) Assume Suitable data if necessary.

- Q1) a) A series R-L circuit with initial current I_0 in the inductor is connected to a d.c. voltage V at $t = 0$. Derive the expression for the instantaneous current through the inductor for $t > 0$. [7]
- b) Find current $i(t)$ through inductor using conventional method. The switch is closed at time $t = 0$. Refer fig. no. 1. [5]

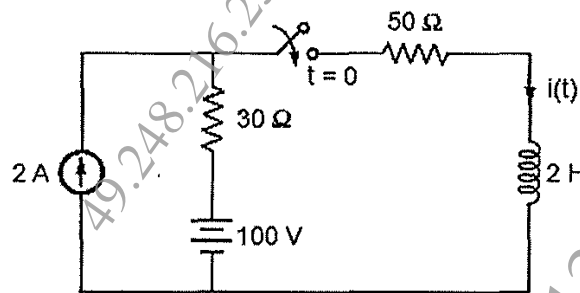


Fig. No. 1

- c) Obtain the expression for current in series RL circuit connected to a d. c. voltage V for $t > 0$. Assume initial current through inductor as zero. [5]

OR

P.T.O.

- Q2) a)** What is time constant? Explain time constant in case of series R-L and series R-C circuit. [7]
- b)** A series R-C circuit shown in fig.2 consists of $R = 10 \text{ ohm}$ and $C = 0.1 \text{ F}$. Initially switch K is kept open for very long time. At $t = 0$ it is closed. Find the expression for $v_c(t)$. [10]

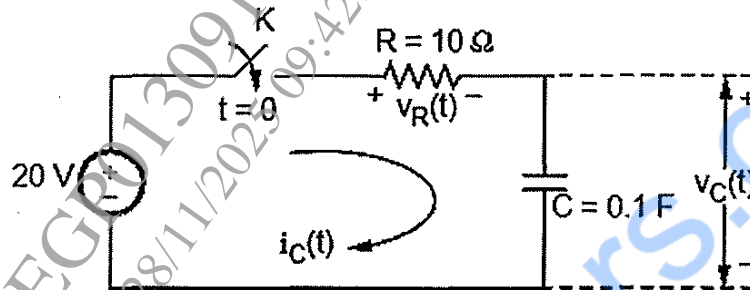


Fig.No.2

- Q3) a)** Explain the properties of Laplace Transform. [6]
- b)** Obtain inverse Laplace transform of [6]

$$F(s) = \frac{1}{s(s+2)}$$

by using convolution integral.

- c)** Explain advantages and disadvantage of Laplace transform. [6]

OR

- Q4) a)** Define and explain the characteristics if [6]
- Unit step function
 - Unit ramp function
 - Unit impulse function
- b)** Find the Laplace transform of $\cos \omega t$. [6]
- c)** Obtain $F(s)$ for the signal shown in fig. no. 3. Also determine its Laplace transform. [6]

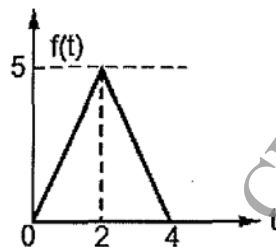


Fig. No. 3

- Q5) a) Express z-parameters in terms of y-parameters. [9]
 b) Find Y parameters of the network shown in figure no. 4 [8]

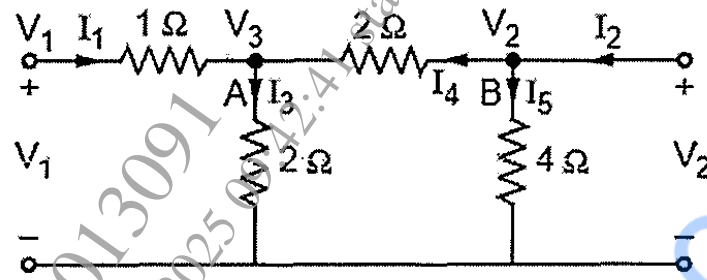


Fig. No. 4

OR

- Q6) a) What is low pass filter? Derive the expression for the cut-off frequency of prototype low pass filter in terms of L and C. [9]
 b) Design a prototype low pass filter sections if design impedance $R_0 = 500$ ohm and cut-off frequency $f_c = 2$ kHz. [8]
- Q7) a) Explain the necessary conditions for transfer function. [9]
 b) Find the network functions $Z_{11}(s)$ and $Z_{21}(s)$ for the network shown in fig. No.5. [9]

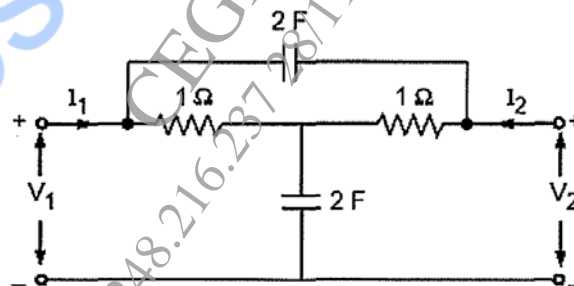


Fig. No. 5

OR

- Q8) a) Explain the significance of poles and zeros. [9]
 b) How to obtain time domain behaviour from a pole-zero plot? [9]
