

Total No. of Questions : 4]

SEAT No. :

PF201

[Total No. of Pages : 2

APR-26/SE/Insem-247

S.E. (Electrical Engineering) (Insem)

ELECTRICAL MACHINES-I

(2019 Pattern) (Semester - IV) (203146)

Time : 1 Hour]

[Max. Marks : 30

Instructions to the candidates:

- 1) *Solve Q.1 or Q.2 and Q.3 or Q.4.*
- 2) *Figures to the right side indicate full marks.*
- 3) *Neat diagrams must be drawn wherever necessary.*
- 4) *Assume suitable data if necessary.*
- 5) *Use of non-programmable calculator is allowed.*

Q1) a) What are the losses taking place in the transformer? Derive the condition for maximum efficiency of the transformer. [7]

b) What is an autotransformer? Derive the equation for the saving of copper in the case of autotransformer as compared to two winding transformers along with the necessary diagram. [8]

OR

Q2) a) With neat circuit diagram explains open circuit and short circuit tests on a single-phase transformer for finding the voltage regulation and efficiency of the transformer. [7]

b) Sketch and explain the phasor diagram of the single-phase transformer at the ON load considering the effect of winding resistance and magnetic leakage. [8]

Q3) a) With proper connection and phasor diagrams describe the star/star connection of the three-phase transformer. Explain it in brief. [7]

b) Two 100-kW, single-phase transformers are connected in parallel both on the primary and secondary. One transformer has an ohmic drop of 0.5% at full-load and an inductive drop of 8% at full-load current. The other has an ohmic drop of 0.75% and inductive drop of 2%. Show how will they share a load of 180 kW at 0.9 power factor. [8]

OR

P.T.O.

Q4) a) With the neat sketch and phasor diagram explain the V-V connection of the transformer. [7]

b) State the necessity of parallel operation of the transformer. State any four necessary conditions for satisfactory parallel operation of the transformer. [8]

❧ ❧ ❧