

APR-26/SE/Insem-248

S.E. (Electrical Engineering) (Insem)

NETWORK ANALYSIS

(2019 Pattern) (Semester-IV) (203147)


Time : 1 Hour]

[Max. Marks : 30


Instructions to the candidates:

- 1) Answer Q.1 or Q.2 and Q.3 or Q.4.
- 2) Neat diagrams must be drawn wherever necessary.
- 3) Figures to the right indicate full marks.
- 4) Use of non-programmable calculator is allowed.
- 5) Assume suitable data, if necessary.

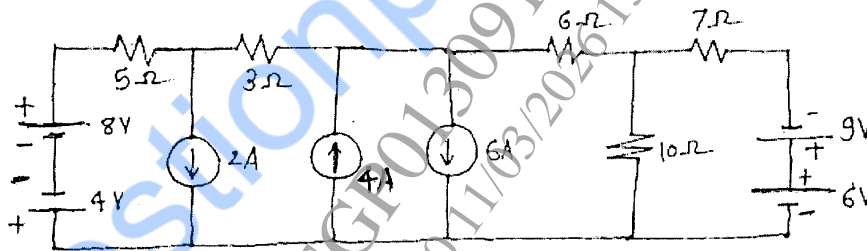Q1) a) Using Source Transformation, calculate power dissipated in 10Ω resistor in the circuit below. [7]




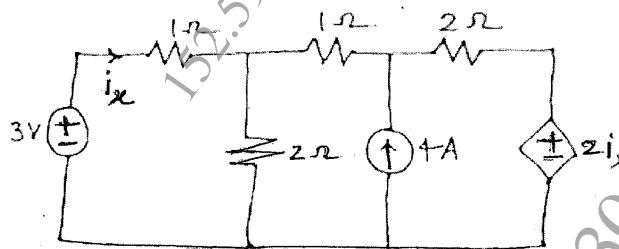b) Find current i_x in the circuit below using Mesh Analysis. [8]




OR

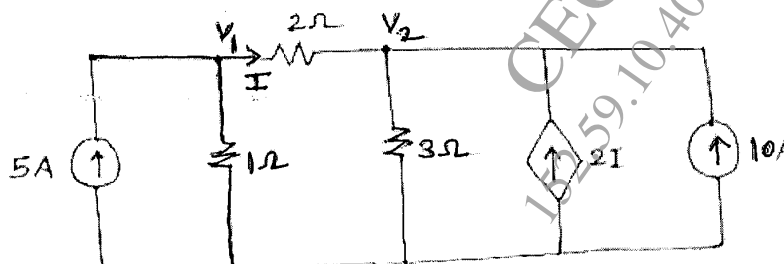Q2) a) Find voltages V_1 and V_2 using Nodal Analysis. [7]




P.T.O.

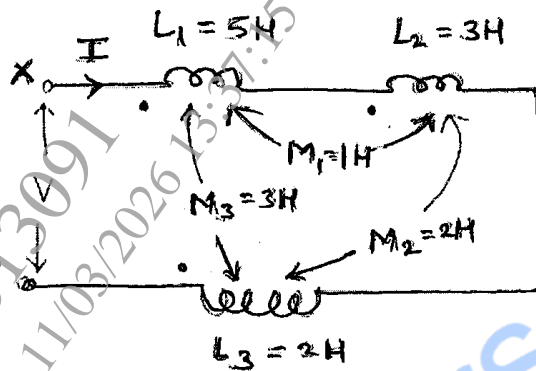
- b) Calculate effective inductance between terminals X and Y for the circuit below: [8]



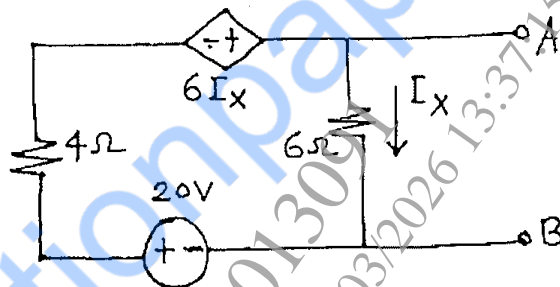- Q3) a) What resistance connected between A & B will receive maximum power? Also, find the value of maximum power that will be delivered. [7]




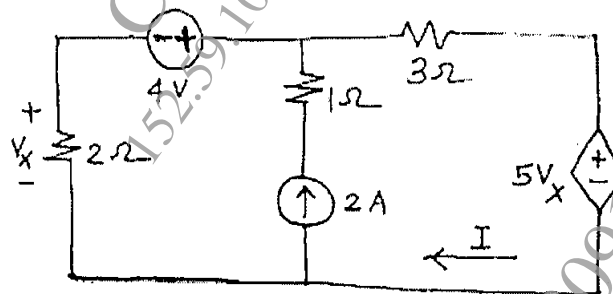- b) State Superposition Theorem and hence find current I using Superposition Theorem. [8]



OR

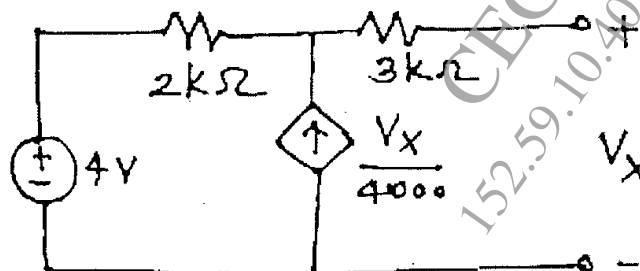- Q4) a) Obtain Thevenin's equivalent circuit of the network below. [7]



- b) State Reciprocity Theorem and hence verify it for the circuit below by considering current source as excitation and voltage V_c as response. [8]

