

Total No. of Questions :10]

SEAT No. :

P3608

[5560]-563

[Total No. of Pages : 2

T.E. (Electrical)
POWER ELECTRONICS
(2015 Pattern) (Semester - I)

Time : 2½ Hours]

[Max. Marks : 70

Instructions to the candidates:

- 1) *Answer any one questions from Q1 & Q2, Q3 & Q4, Q5 & Q6, Q7 & Q8, Q9 & Q10*
- 2) *Neat diagrams must be drawn wherever necessary.*
- 3) *Black figures to the right indicate full marks.*
- 4) *Assume suitable data if necessary.*

- Q1) a)** Explain with neat circuit diagram operation of R-C triggering circuit of Thyristor **[5]**
- b)** Write short note on Class E Chopper. **[5]**

OR

- Q2) a)** Describe working of single phase semi converter with RL load. Draw waveforms of load voltage, load current. **[5]**
- b)** Draw and explain output and transfer characteristics of MOSFET **[5]**

- Q3) a)** Describe working of single phase circulating type of dual converter with output voltage waveform. **[5]**
- b)** State and explain different modes of operation of SCR with the help of V-I characteristic. **[5]**

OR

- Q4) a)** Explain the following ratings of the thyristor.
- i) Latching current
 - ii) Holding current **[5]**
- b)** For a type A chopper circuit, source voltage $V_s = 220V$, chopping period, $T = 2000 \mu s$, on period $= 600 \mu s$, load circuit parameters: $R = 1\Omega$, $L = 5mH$ and $E = 24V$. Calculate the maximum and minimum values of steady state output current. **[5]**

P.T.O.

- Q5) a)** With neat diagram explain four mode operation of a TRIAC. [8]
- b)** Explain working of three phase fully controlled converter with RL load & firing angle of 30° . Draw output voltage waveforms & obtain expression for phase voltage & Line voltage. [8]

OR

- Q6) a)** A three phase full converter operating from three phase, 415V, 50Hz supply with resistive load, Determine average output voltage for $\alpha = 30^\circ$ and $\alpha = 90^\circ$. [8]
- b)** What is two stage ac voltage regulator? Explain its operation with output waveform for RL Load. [8]

- Q7) a)** For single pulse width modulation with quasi square wave show that output voltage can be expressed as
$$V_0 = \sum_{n=1,3,5,\dots}^{\infty} \frac{4V_s}{n\pi} \sin \frac{n\pi}{2} \sin n\omega t$$
 Where V_s is source voltage and pulse width is $2d$. [8]

- b)** Explain with circuit diagram and waveforms operation of single phase current source inverter. [8]

OR

- Q8) a)** Explain Sinusoidal Pulse width modulation with necessary waveforms. [8]

- b)** A single phase full bridge inverter is operated from 48V battery and is supplying power to a pure resistive load of 10Ω . Determine [8]

- i) Output voltage (rms voltage)
- ii) Output rms power

- Q9) a)** List different harmonic elimination techniques used in inverter. Explain any two methods in detail. [10]

- b)** Draw a neat diagram and explain cascaded multi level converter. [8]

OR

- Q10) a)** Explain working of three phase six step voltage source inverter in 180° mode of operation. For star connected load draw output voltage waveforms. Show devices conducting in each step. [10]

- b)** Write short note on Flying Capacitor multilevel converter. [8]

