

Total No. of Questions : 4]

SEAT No. :

PC34

[6360]-34

[Total No. of Pages : 1

T.E. (Electrical Engineering) (Insem)

POWER ELECTRONICS

(2019 Pattern) (Semester- I) (303142)

Time : 1 Hour]

[Max. Marks : 30

Instructions to the candidates:

- 1) Solve Q1 or Q2; Q3 or Q4.
- 2) Figures to the right indicate full marks.
- 3) Neat diagrams must be drawn wherever necessary.
- 4) Assume suitable data if necessary.
- 5) Use of non-programmable calculator is allowed.

Q1) a) Draw & explain switching characteristics of SCR. [7]

b) Explain four modes of operation of TRIAC. [8]

OR

Q2) a) Explain over voltage & over current protections for SCR. [7]

b) Define the following terms in SCR. [8]

- i) Forward break over voltage
- ii) Latching current
- iii) Holding current
- iv) I^2t rating

Q3) a) Draw VI characteristics of MOSFET & explain its control. [7]

b) Explain Class E chopper feeding RLE load in detail. [8]

OR

Q4) a) What is time ratio control in dc chopper? Explain the use of TRC for controlling the output voltage in choppers. [7]

b) Explain with a diagram step up chopper and derive the expression for the output voltage. A step up chopper with a pulse width of 150 ms is operating at 220 V dc supply. Compute the load voltage if the blocking period of the device is 40 ms. [8]

