

Total No. of Questions : 4]

SEAT No. :

PE33

[6579]-334

[Total No. of Pages : 1

T.E. (Electrical Engineering) (Insem)
POWER ELECTRONICS
(2019 Pattern) (Semester - I) (303142)

Time : 1 Hour]

[Max. Marks : 30

Instructions to the candidates:

- 1) Solve Q.1 or Q.2, Q.3 or Q.4.
- 2) Figures to the right indicate full marks.
- 3) Neat diagrams must be drawn wherever necessary.
- 4) Assume suitable data, if necessary.
- 5) Use of electronic packet calculator and smith chart is allowed.

- Q1) a)** Describe different protections provided to SCR against [7]
- i) Over voltage
 - ii) Overcurrent
 - iii) dv/dt
 - iv) di/dt
 - v) Thermal
- b) Define following term with respect to SCR and show them on VI and Turn on Characteristics. [8]
- i) Latching Current
 - ii) Holding Current
 - iii) delay time
 - iv) rise time

OR

- Q2) a)** Draw neat diagram of class D commutation and explain its working. [7]
- b) Explain four mode operation of TRIAC. [8]
- Q3) a)** With neat constructional diagram, explain operation of MOSFET. Draw Output and transfer characteristics of MOSFET. [7]
- b) List different voltage control techniques of chopper. Explain any two in detail. [8]

OR

- Q4) a)** A chopper circuit is operating on a TRC control mode at a frequency of 2kHz on a 230V dc supply. For output voltage of 170V, find conduction and blocking period of the step down chopper. [7]
- b) What is four quadrants (class E) operation of chopper? Describe with diagram operation of it in each quadrant. [8]