

Total No. of Questions : 4]

SEAT No. :

**PB272**

**[6270]-60**

[Total No. of Pages : 2

**B.E. (Electrical Engineering) (Insem)  
SWITCHGEAR & PROTECTION  
(2019 Pattern) (Semester - VIII) (403148)**

*Time : 1 Hour]*

*[Max. Marks : 30*

*Instructions to the candidates:*

- 1) *Solve Q.1 or Q.2, Q.3 or Q.4.*
- 2) *Figures to the right indicate full marks.*
- 3) *Neat diagrams must be drawn wherever necessary.*
- 4) *Assume suitable additional data if necessary.*
- 5) *Use of non-programmable calculator is allowed.*

**Q1) a)** Explain different causes of faults in a power system. **[3]**

b) Define zones of protection? Explain primary and backup protection with diagrams? **[6]**

c) An IDMT overcurrent relay has a current setting of 175% and a time multiplier setting of 0.5. The relay is connected to supply circuit through a CT having ratio 400/5. Calculate the time of operation of relay if the circuit carries a fault current of 7000A. At TMS = 1, operating time at various PSM are given below **[6]**

PSM	2	4	5	8	10	20
Operating time in Sec.	10	5	4	3	2.8	2.4

OR

**Q2) a)** Explain with neat diagram principle of current differential relay. **[3]**

b) With a suitable diagram explain construction & working of Induction disc type overcurrent relay? **[6]**

c) Explain the trip circuit of C.B with suitable diagram? **[6]**

**P.T.O.**

- Q3) a)** Explain high and low resistance principles of arc interruption in case of circuit breakers? [8]
- b)** Derive the equation for restriking voltage, RRRV & maximum value of RRRV in case of circuit breaker. [7]

OR

- Q4) a)** A 3 phase 50 Hz alternator has inductance of 3 mH/ph & capacitance of 0.025  $\mu$ F/ph. The circuit breaker opens when RMS current is 8000 A. Determine: [8]
- i) frequency of oscillations
  - ii) Peak restriking voltage
  - iii) Average rate of restriking voltage
  - iv) Maximum value of restriking voltage
- b)** Explain with suitable diagrams resistance switching in case of circuit breaker? State the expression for damped frequency oscillations. [7]

\* \* \*