

Total No. of Questions : 8]

SEAT No. :

PD-5277

[Total No. of Pages : 2

[6402]-23R

**S.E. (Electronics & Computer) (Electronics/E&TC)**  
**(Electronics-VLSI Design & Technology/**  
**Electronics & Comm.-(A.C.T.))**

**DIGITAL CIRCUITS**

**(2019 Pattern) (Semester - III) (204182)**

*Time : 2½ Hours]*

*[Max. Marks : 70*

*Instructions to the candidates:*

- 1) *Answer Q.1 or Q.2, Q.3 or Q.4, Q.5 or Q.6, Q.7 or Q.8 .*
- 2) *Neat diagrams must be drawn wherever necessary.*
- 3) *Figures to the right indicate full marks.*

- Q1)** a) Design a full adder using 2 half adders. [7]
- b) Design and implement one bit comparator. [5]
- c) Design 16:1 multiplexer using two 8:1 multiplexer. [5]

OR

- Q2)** a) Design and explain 1:4 DEMUX with block diagram, truth-table, equation and logic diagram. [7]
- b) Implement the full subtractor using a 1:8 demultiplexer. [5]
- c) Draw and explain the look-ahead carry generator. [5]

- Q3)** a) Design a sequence generator using T FFs for sequence 1101. [8]
- b) Distinguish between synchronous counter and asynchronous counter. [5]
- c) Explain with diagram the working of D type Flip-flop. Give its truth table. [5]

OR

**P.T.O.**

- Q4)** a) Draw and explain 3 bit asynchronous counter using JK FF. [8]  
b) Design a 3 bit twisted ring counter. Draw logic diagram. [5]  
c) Compare Moore and Mealy machines. [5]

- Q5)** a) What do you mean by excitation table of flip flop? Write the excitation table of [9]  
i) D flip flop  
ii) J-K flip flop  
b) Explain : [8]  
i) State Table  
ii) State Diagram  
iii) State Assignment  
iv) ASM chart

OR

- Q6)** a) Design a sequence detector to detect a sequence 1101 using D FF (Use Moore machine) [9]  
b) Explain in short:  
i) Moore Machine  
ii) Mealy Machine [8]

- Q7)** a) Explain block diagram of FPGA with its basic characteristics. [8]  
b) Write short notes on memories. [10]

OR

- Q8)** a) Implement following Boolean function using PAL. [8]  
 $F1 = \Sigma m (0, 2, 3, 4, 5, 6, 7, 8, 10, 11, 15)$   
 $F2 = m \Sigma (1, 2, 8, 12, 13).$   
b) Describe with neat diagram AND-OR structure of PLA and PAL. [10]

