

Total No. of Questions—8]

[Total No. of Printed Pages—2

Seat No.	
-------------	--

[5559]-137

**S.E. (E & TC/Electronics) (I Sem.) EXAMINATION, 2019**  
**DIGITAL ELECTRONICS**  
**(2015 PATTERN)**

**Time : Two Hours**

**Maximum Marks : 50**

*Instructions to the candidates:*

- 1) Attempt Q.1 or Q.2, Q.3 or Q.4, Q.5 or Q.6, Q.7 or Q.8.
- 2) Neat diagrams must be drawn wherever necessary.
- 3) Figures to the right indicate full marks.
- 4) Assume suitable data, if necessary.
- 5) Use of logarithmic tables, slide rule and electronic non programmable calculator is allowed.

- Q1 a. Design 3 bit binary to grey code converter 06  
b. Convert D F/F to J/K F/F 06
- OR
- Q2 a. Design Even bit parity checker 06  
b. Design 3 bit twisted ring counter 06
- Q3 a. Design sequence detector to detect..10110.. 06  
b. Give comparisons between TTL, ECL and CMOS logic families 04  
c. Draw and explain SR Flip Flop using NAND gates. 02
- OR
- Q4 a. Draw and explain TTL to CMOS interface. 06  
b. Compare Moor and Mealy Machine 04  
c. What is Clock Skew and C'lock jitter? 02
- Q5 a. Implement following using PLA 06  
F1 =  $AB'+AC+A'BC'$   
F2 =  $(AC+BC)$   
b. List Various semiconductor memory with their characteristic. 07

P.T.O.

- OR
- Q6 a Explain PROM with diagram 06  
b List Various Programmable logic Devices with their characteristic 07
- Q7 a List & explain Mode of Timer/ Counter for 8051 05  
b Write short note on 8051 feature 04  
c Mention any four addressing modes of 8051? 04
- OR
- Q8 a Draw and explain Program Status Word 05  
b Compare Microcontroller & Microprocessor 04  
c Explain the Instruction for arithmetic's with examples 04