

Total No. of Questions : 8]

SEAT No. :

PA-1190

[Total No. of Pages : 2

[5925]-212

S.E. (E & TC/Electronics)

ELECTRONIC & CIRCUITS

(2019 Pattern) (Semester-III) (204181)

Time : 2½ Hours]

[Max. Marks : 70

Instructions to the candidates:

- 1) Attempt Q.No.1 or Q.No.2, Q.No.3 or Q.No.4, Q.No.5 or Q.No.6, Q.No.7 or Q.No.8.
- 2) Figures to the right indicate full marks.
- 3) Assume suitable data, if necessary.
- 4) Neat diagrams must be drawn wherever necessary.

- Q1)** a) Explain with diagram the operation of an adjustable voltage regulator using IC LM 317. [7]
- b) Design the adjustable voltage regulator for the following specification  
output voltage = 5V – 10V  $I_0 = 1.2$  A,  $I_{adj} = 100\mu$ A,  $R_1 = 240\Omega$ . [7]
- c) What is SMPS? Explain working principle of it. [4]

OR

- Q2)** a) Draw and explain the block diagram of LM 337 and list the specification of it? [7]
- b) Determine the range of output voltage for adjustable voltage regulator LM317 for  $R_1 = 240\Omega$ ,  $R_2 = 4.7$  k $\Omega$  Assume  $I_{adj} = 100$   $\mu$ A. [7]
- c) Which are the factor that affect on the output of the voltage regulator? [4]

- Q3)** a) List different configuration of differential amplifier and explain dual input dual output in details? [7]
- b) Define the characteristics of op-amp [6]
- i) Input bias current
  - ii) Slew rate
  - iii) CMRR
- c) Find the 'Q' point for a dual input balanced output differential amplifier with  $R_C = R_E = 65$  k $\Omega$ . supply voltage used is  $\pm 1$ s V. [4]

OR

P.T.O.

- Q4)** a) Explain the need of level shifting stage in op-amp. Explain any one circuit for the same. [7]
- b) Draw and explain voltage series feedback amplifier and list their advantages. [6]
- c) Explain the concept of current mirror circuit? [4]

- Q5)** a) Draw an inverting summing amplifier with three inputs and derive expression for its output voltage  $V_o$ ? [8]
- b) Design a practical integrator with input signal of 2VPP and cutoff frequency of 2.5 kHz. for DC voltage gain to 10. [6]
- c) Explain with diagram the concept of voltage follower circuit using op-amp. [4]

OR

- Q6)** a) Draw and explain an Instrumentation amplifier interface with RTD bridge for temperature measurement. [8]
- b) Using IC 741 op-amp with supply voltage of  $\pm 15V$  design an inverting schmitt trigger circuit to have  $V_{UTP} = +3V$ ,  $V_{LTP} = -3V$ . [6]
- c) What is the difference between inverting and non-inverting amplifier. [4]

- Q7)** a) Classify different types of ADC and explain iwth diagram dual scope ADC. [6]
- b) Calculate the O/P voltage for a DAC whose output range is 0 to 10 V and input binary number 1001. [6]
- c) Explain various specification of ADC. [5]

OR

- Q8)** a) Explain with neat diagram the register weighted and R-2R DAC? [6]
- b) For on 10 bit successive approximation type A/D converter driven by a 2MHz clock, find the conversion time? [6]
- c) Draw and explain V to I convertor. [5]

