

Total No. of Questions : 6]

SEAT No. :

PA-423

[Total No. of Pages : 2

[5931]-8

S.E. (Electronics/E&TC/Electronics & Computer)

DIGITAL CIRCUITS

(2019 Pattern) (Semester - I) (204182)

Time : 1 Hour]

[Max. Marks : 30

Instructions to the candidates:

- 1) Answer Q.1 or Q.2, Q.3 or Q.4, Q.5 or Q.6.
- 2) Figures to the right indicate full marks.
- 3) Neat diagrams must be drawn wherever necessary.
- 4) Use of non-programmable calculator allowed.
- 5) Assume suitable data, if necessary.

Q1) a) Explain the following characteristics of digital IC's. [6]

- i) Figure of Merit
- ii) Propagation delay
- iii) V_{IH} and V_{OH}

b) Draw and explain the working of CMOS Inverter. [4]

OR

Q2) a) Draw and explain the working of 2-input TTL NAND gate. List advantages of Totem Pole. [6]

b) Explain the following characteristics of digital IC's. [4]

- i) Noise Margin
- ii) Fan out and fan in

Q3) a) Design full adder using logic gates. [4]

b) Minimize the following expression using K-map and implement using logic gates : $Y = \sum m (1, 3, 5, 9, 11, 13)$. [6]

OR

P.T.O.

- Q4)** a) Design 3-bit Gray code to Binary converter. [6]
b) Design full subtractor using logic gates. [4]

- Q5)** a) Minimize the following function using K-map and implement it using only NAND gates. $F(P, Q, R, S) = \sum m(4, 5, 6, 7, 8, 12) + d(1, 2, 3, 9, 11, 14)$ [6]
b) Compare TTL and CMOS logic families. [4]

OR

- Q6)** a) Explain the current parameters in TTL logic. [4]
b) Minimize the following function using Quine Mc Clusky method. $F(A, B, C, D) = \sum \pi(0, 3, 5, 7, 12, 15) + d(2, 9)$. [6]

