

Total No. of Questions : 8]

SEAT No. :

**P1485**

[Total No. of Pages : 2

[6002]-112

**S.E. (Electronics/ E&T.C)**

**ELECTRONIC CIRCUITS.**

**(2019 Pattern) (Semester-III) (204181)**

*Time : 2½ Hours]*

*[Max. Marks : 70*

*Instructions to the candidates:*

- 1) Answer Q.1 or Q.2, Q.3 or Q.4, Q.5 or Q.6, Q.7 or Q.8.
- 2) Figure to the right indicate full marks.
- 3) Neat diagrams must be drawn wherever necessary.
- 4) Assume suitable additional data, if necessary.
- 5) Use of non-programmable calculator is allowed.

- Q1) a)** Draw block diagram of regulated power supply and explain the function of each block? [6]
- b) With the help of neat diagram explain buck-boost converter? [6]
- c) Draw and explain low dropout regulator? [6]

OR

- Q2) a)** Design a regulated power supply using LM 317 for output voltage  $V_o$  and  $I_{Adj}=100 \mu A$ . [6]
- b) Explain the working of SMPS with neat diagram? [6]
- c) Compare regulated and unregulated power supply? [6]

- Q3) a)** List all parameter's of op-amp. Explain any four in brief ? [6]
- b) Explain significance of negative feed back, in op-amp amplifier? [5]
- c) A dual input balanced output differential amplifier has following specification  $R_c=2.7K\Omega$ ,  $R_E=4.5k\Omega$ ,  $\pm V_{CC}=\pm 10v$ ,  $\beta=100$ ;  $V_{BE}=0.7V$ ;  $r_e=26.34\Omega$  calculate [6]

- i) Voltage gain ( $A_d$ )
- ii)  $R_{in}$
- iii)  $R_o$

OR

- Q4) a)** Draw block diagram of op-amp and explain each block? [6]
- b) Compare inverting and non-inverting configuration of op-amp with following parameters:
- i) Feedback Type
  - ii)  $R_i$
  - iii) Gain
  - iv) Bandwidth [5]

**P.T.O.**

- c) Determine the Q point for dual input and balanced output differential amplifier with  $R_C=R_E=65K\Omega$  and supply voltage  $\pm 15V$  assume suitable data. [6]

- Q5)** a) Draw an inverting summing amplifier with three input and derive expression for the output voltage  $V_o = -(V_a+V_b+V_c)$  [6]  
b) Design a practical Integrator with input Signal of 1.5 vpp and cut off frequency of 3KHz for DC voltage gain of 10. [6]  
c) Draw circuit diagram of 30p-amp Instrumentation amplifier and write its o/p equation? [6]

OR

- Q6)** a) With the help of neat diagram explain working of symmetrical schmitt trigger? [6]  
b) Design a square wave generater using op-amp for frequency 1KHz to 10 KHz with 50 % duty cycle. draw diagram with component value. [6]  
c) Explain practical differentiator circuit with neat diagram? list limitations of ideal differentiator? [6]

- Q7)** a) Explain voltage to current converter with floating load? [6]  
b) Determine the output voltage produced by 4 bit R-2R ladder DAC with  $V_{ref}=5v$  for bit sequence i) 0110 ii) 1101 [5]  
c) Explain working of flash ADC in details. [6]

OR

- Q8)** a) Define terms. [6]  
i) Lock range  
ii) Capture range.  
iii) Pull in time  
iv) Free running frequency.  
b) With the neat diagram explain working of weighted resistor DAC? [6]  
c) Find the digital output of an ADC having  $t_1=83.33$  Msec and  $V_R=100$  mv for an input voltage. of +100mV. The clock frequency is kHz [5]

