

Total No. of Questions : 8]

SEAT No. :

PB3621

[6261]-26

[Total No. of Pages : 2

**S.E. (Electronics /E&TC)
ELECTRONIC CIRCUITS**

(2019 Pattern) (Semester-III) (204181)

Time : 2½ Hours]

[Max. Marks : 70

Instructions to the candidates:

- 1) *Attempt Q1 or Q2, Q3 or Q4, Q5 or Q6, Q7 or Q8.*
- 2) *Figures to the right indicate full marks.*
- 3) *Assume suitable data if necessary.*
- 4) *Neat diagrams must be drawn wherever necessary.*

- Q1)** a) Define Voltage regulation. Explain the any three performance parameters of voltage regulator. **[6]**
- b) IC Voltage Regulator using IC 317, Calculate values of R2 for the output voltage 10v to 20v, assume R1= 240 Ω and Iadj = 100μA. **[6]**
- c) Compare Linear power supply and Switch Mode Power Supply (SMPS). **[6]**

OR

- Q2)** a) Draw and explain the block diagram of Power Supply. **[6]**
- b) IC Voltage Regulator using IC 317, Calculate values of R2 for the output voltage 5v to 10v, assume R1= 240 Ω and Iadj = 100μA. **[6]**
- c) Write a Short note on “Low drop out Voltage regulator”. **[6]**

- Q3)** a) Draw Block diagram of OP - AMP. and explain the function of each block. **[5]**
- b) Define the following Characteristics of OPAMP **[6]**
- i) Input offset voltage
 - ii) Slew Rate
 - iii) CMRR (Common Mode Rejection Ratio)
- c) Compare Concept of Voltage Series and Voltage Shunt in OP AMP. **[6]**

OR

P.T.O.

- Q4)** a) List types of differential amplifiers. Draw dual input balanced output differential amplifier. [5]
- b) State Ideal and Typical values of OP AMP parameters (IC 741). [6]
- c) Explain with circuit diagram necessity of level shifting in OP AMP. [6]

- Q5)** a) Draw and explain Inverting amplifier. Draw its input and output waveforms. [6]
- b) Design a Practical differentiator circuit for the input signal having maximum frequency of operation 250 Hz. [6]
- c) Draw and explain Inverting Schmitt trigger circuit using OP AMP. [6]

OR

- Q6)** a) Compare Inverting and Non-Inverting amplifier in OP AMP. [6]
- b) Design a Practical Integrator circuit to operate at $f=4$ KHz and gain equal to 4. [6]
- c) Draw and explain square wave Generator using OP AMP. [6]

- Q7)** a) Draw and explain V to I Converter using grounded load using OP AMP. [5]
- b) Draw and explain the circuit of R/2R DAC using OP AMP. [6]
- c) With the help of neat block diagram explain operation of PLL. [6]

OR

- Q8)** a) Draw and explain I to V Converter using OP AMP. [5]
- b) Draw and explain the circuit of binary weighted resistor DAC using OP AMP. [6]
- c) Define the following specifications of ADC [6]
- Resolution
 - Accuracy
 - Conversion time

