

Total No. of Questions—8]

[Total No. of Printed Pages—3

Seat No.	
-------------	--

[5252]-536

S.E. (E&TC/Electronics) (Second Semester) EXAMINATION, 2017

INTEGRATED CIRCUITS

(2015 PATTERN)

Time : Two Hours

Maximum Marks : 50

N.B. :— (i) Answer Q. 1 or Q. 2, Q. 3 or Q. 4, Q. 5 or Q. 6 and Q. 7 or Q. 8.

(ii) Neat diagrams must be drawn wherever necessary.

(iii) Figures to the right side indicate full marks.

(iv) Use of calculator is allowed.

(v) Assume suitable data if necessary.

1. (a) Justify, how constant current source is used in place of R_E to improve CMRR for differential amplifier. [6]

(b) Draw neat circuit diagram of three Op-amp Instrumentation amplifier and derive its output equation. [6]

Or

2. (a) An emitter biased Dual input balanced output differential amplifier has the following specifications :

$V_{CC} = \pm 10$ V, $R_{C1} = R_{C2} = 3.7$ k Ω and $R_E = 4.2$ k Ω ,
 $\beta_{ac} = \beta_{dc} = 100$ & $V_{BE} = 0.7$ V. Calculate : [6]

(1) Voltage Gain (Ad)

(2) Input Resistance (Ri)

(3) Output Resistance (Ro).

P.T.O.

- (b) Draw the circuit diagram of Practical differentiator along with frequency response and explain its operation. [6]
3. (a) Explain with a neat circuit diagram working of inverting precision full wave rectifier with its waveform. [6]
- (b) With neat circuit diagram, explain voltage to current converter with grounded load. [6]
- Or*
4. (a) Draw and explain circuit of Sample and Hold circuit using Op-amp with its waveform. [6]
- (b) The output of 8-bit ADC with all 1's when $V_i = 5 \text{ V}$, find its :
- (1) Resolution
- (2) Digital output code, If $V_i = 1.7 \text{ V}$. [6]
5. (a) Define the term "Lock range", "Capture range" and "Free running frequency" and explain transfer characteristics of PLL. [7]
- (b) Design a first order low pass filter with higher cut-off frequency of 1 kHz with pass gain '2'. Draw the designed circuit diagram. Assume $C = 0.1 \mu_f$ and $R_f = 10 \text{ k}\Omega$. [6]
- Or*
6. (a) With the help of neat circuit diagram explain the operation of Wien bridge oscillator. [6]

(b) Design a wide bandpass filter having $f_L = 400$ Hz, $f_H = 2$ kHz and pass band 4. Also calculate the bandwidth. [7]

Assume : $C' = 0.01 \mu\text{f}$ and $C = 0.05 \mu\text{f}$

$R_1' = 10 \text{ k}\Omega$ and $R_1 = 10 \text{ k}\Omega$

7. (a) Calculate output frequency ' f_o ', Lock range ' Δf_L ', Capture range ' Δf_c ' of a PLL, If $R_T = 1 \text{ k}\Omega$, $C_T = 0.1 \mu\text{f}$, filter capacitor $C = 1 \mu\text{f}$ and internal resistance = $3.6 \text{ k}\Omega$. Assume $\pm V = 10\text{V}$. [6]

(b) Design all pass filters with a phase shift of -135° . At a frequency of 2 kHz at the output. Draw detailed designed circuit diagram. Assume $C = 0.1 \mu\text{f}$ and $R_1 = 10 \text{ k}\Omega$. [7]

Or

8. (a) Write short notes on application of PLL : [6]

(1) Frequency Multiplier

(2) FM Demodulator.

(b) Design a first order high pass filter with higher cut-off frequency of 10 kHz with pass gain '1.5'. Draw the designed circuit diagram. Assume $C = 0.01 \mu\text{f}$ and $R_1 = 10 \text{ k}\Omega$. [7]