

Total No. of Questions—8]

[Total No. of Printed Pages—2

Seat No.	
-------------	--

[5459]-138

S.E. (ELECTRONICS/E&TC) (II Sem.) EXAMINATION, 2018

INTEGRATED CIRCUITS

(2015 PATTERN)

Time : Two Hours

Maximum Marks : 50

N.B. :— (i) Neat diagrams must be drawn wherever necessary.

(ii) Your answers will be valued as a whole.

(iii) Assume suitable data, if necessary.

1. (a) Draw block diagram of op-amp and explain in detail. [6]

(b) Draw neat circuit diagram of :

(i) Non-inverting amplifier. [2]

(ii) Inverting summing amplifier. [4]

Or

2. (a) Write notes on : [6]

(i) Level shifter

(ii) Current mirror circuits.

(b) Draw neat circuit diagram of : [6]

(i) Voltage follower

(ii) Single op-amp difference amplifier.

3. (a) Draw circuit diagram of inverting symmetrical Schmitt trigger and plot hysteresis and explain in short. [6]

(b) Draw V to I converter with grounded load and explain with its output equation. [6]

P.T.O.

Or

4. (a) Draw circuit diagram of precision full wave rectifier with showing input and output waveform. [6]
(b) Draw V to I converter with floating load and explain with its output equation. [6]
5. (a) Define the term Free running frequency, Lock range and Capture range in PLL. [6]
(b) Explain the operation of Wein bridge oscillator with neat circuit diagram. [7]

Or

6. (a) Explain PLL with its block diagram. [6]
(b) Draw circuit diagram of phase shift oscillator and explain its operation. [7]
7. (a) Design wide band pass filter having $F_L = 1$ kHz and $F_h = 6$ kHz with pass band gain is 2.
Draw circuit diagram with its component values. [7]
(b) Draw circuit diagram of first order LPF with its frequency response. [6]

Or

8. (a) Design a first order band reject filter for $F_h = 2$ kHz and $F_L = 6$ kHz with pass band gain is 3.
Draw circuit diagram with its component values. [7]
(b) Draw circuit diagram of first order HPF with its frequency response. [6]