

Total No. of Questions : 8]

SEAT No. :

P1727

[Total No. of Pages : 3

[5460] - 556
T.E. (E & TC)
POWER ELECTRONICS
(2015 Pattern)

Time : 2½ Hours]

[Max. Marks : 70

Instructions to the candidates:

- 1) *Neat diagrams must be drawn wherever necessary.*
- 2) *Use of logarithmic tables slide rule, Mollier charts, electronic pocket calculator and steam tables is allowed.*
- 3) *Assume suitable data, if necessary.*

- Q1)** a) Explain the gate drive circuit requirements for MOSFET & draw the sample drive circuit. **[6]**
- b) Explain effect of source impedance on the performance of 1Φ full converter. Derive the expression for average output voltage? **[6]**
- c) In a single phase full converter with highly inductive load is feed from 120 V RMS ac mains & fired at $\alpha = 45$ deg., Calculate **[8]**
- i) Average Load voltage.
 - ii) RMS Load Voltage.
 - iii) Power factor.

OR

- Q2)** a) In a full AC to DC converter, explain the rectification mode & line commutated inverter mode of operation with relevant waveforms. **[7]**
- b) Explain single pulse PWM & Sinusoidal PWM control technique for 1ϕ inverter. **[7]**
- c) Explain the following parameters in relation to ac to dc converters, **[6]**
- i) Displacement factor
 - ii) Harmonic factor.
 - iii) Power factor

P.T.O.

Q3) a) Explain the principle of step up chopper feeding R - L load, with neat diagrams and waveforms of load voltage, load current, voltage across switch & current through switch. Derive the expression of output voltage. [8]

b) Explain the operation of Flyback type SMPS and discuss advantages & limitations. [8]

OR

Q4) a) Explain 4 quadrant operation of chopper for DC motor as a load. [8]

b) Draw & explain the operation of single phase AC voltage controller using SCR or IGBT with necessary waveforms. Derive the expression of RMS voltage at output. [8]

Q5) a) Draw the neat diagram of ZCS resonant converter. Explain the operation through waveforms? [8]

b) In a MOSFET operating in a circuit with $V_{DS} = 25V$ & $I_D = 1A$, the thermal resistance $\theta_{jc} = 1^\circ C/W$, Maximum junction temperature is $125^\circ C$, and ambient temperature is $25^\circ C$, the thermal grease is used between heat sink and device case reduces the $\theta_{cs} = 0.3^\circ C/W$, find the appropriate heat sink. [8]

OR

Q6) a) Draw the neat diagram of ZVS resonant converter. Explain the operation through waveforms? [8]

b) Explain dv/dt , di/dt and snubber circuit protection. [8]

Q7) a) A UPS is driving a load of 200 W with lagging pf of 0.82. The efficiency of the inverter is 85% & the battery voltage is 12 V, Find [6]

i) KVA Rating of inverter

ii) AH rating of battery

- b) Draw and explain the fan regulator using Triac & Diac with waveforms at various circuit points? [6]
- c) What are the methods of speed control of DC motor? Explain the how the speed of the separately excited dc motor can be controlled by DC drive system? [6]

OR

- Q8)** a) What is stepper motor drive? Explain with necessary sequence generation, how it works? [8]
- b) Draw & explain torque speed characteristics of DC drive and explain the constant power & constant speed operation of DC motor? [10]

