

Total No. of Questions—8]

[Total No. of Printed Pages—3

Seat No.	
-------------	--

[5558]-105

F.E. EXAMINATION, 2019
BASIC ELECTRICAL ENGINEERING
(2015 PATTERN)

Time : Two Hours

Maximum Marks : 50

- N.B. :—** (i) Answer Q. 1 or Q. 2, Q. 3 or Q. 4, Q. 5 or Q. 6 and Q. 7 or Q. 8.
- (ii) Neat diagrams must be drawn wherever necessary.
- (iii) Figures to the right indicate full marks.
- (iv) Use of Non-programmable scientific calculator is allowed.
- (v) Assume suitable data, if necessary.

- Q.1** a) Define resistance and state its unit. What is the effect of temperature on resistance of the [i] metallic conductor [ii] alloys and [iii] insulator [06]
- b) Find the induced emf in the coil having inductance of 0.15 H when [i] current of 10 A in the coil is switched off in 0.01 sec. [ii] same current is uniformly reversed in 0.01 sec. [06]

OR

- Q.2** a) Obtain the expression for coefficient of coupling between two magnetically coupled coils. [06]
- b) If the temperature coefficient of resistance for copper wire is 0.00393 per degree Celsius at 20 °C. Find the temperature coefficient of resistance at [i] 50 °C and [ii] 70 °C [06]
- Q.3** a) Obtain the emf equation of 1-phase transformer. [06]
- b) Obtain the expression for RMS value of alternating current in terms of its peak value. [07]

P.T.O.

OR

- Q.4** a) A 80 kVA, 1000/250 V, 1-ph 50 Hz transformer has iron loss of 800 W and full load copper loss 1200 W. Find [i] efficiency at full load and power factor = 0.8 lag. [ii] efficiency at half load and power factor = 1 lag. [06]
- b) The alternating current expression is given by $i = 14.14 \sin(100\pi t)$ Amp. Determine: [i] maximum value of current [ii] RMS value of current [iii] average value of current [iv] form factor [v] peak factor [vi] power consumed when it flows through resistance of 10Ω . [07]
- Q.5** a) Obtain the expression for power, when voltage $v = V_m \sin \omega t$ is applied across R-L series circuit. Draw the circuit diagram and phasor diagram. [06]
- b) State the relation between [i] phase voltage and line voltage [ii] phase current and line current in case of balanced delta connected 3-ph load. Using above relations, obtain the expressions for 3-ph active power and 3-ph reactive power. [06]

OR

- Q.6** a) What is series resonance?. Obtain the expression for resonant frequency. [06]
- b) The series circuit having resistance 5Ω and capacitance $150 \mu\text{F}$ is connected to 1-phase, 200 V, 50 Hz AC supply. Calculate - [06]
- [i] capacitive reactance X_c [ii] impedance [iii] current drawn by the circuit [iv] power factor [v] Active power and [vi] reactive power.
- Q.7** a) Derive the equations to convert Delta connected resistive circuit into equivalent star circuit. [06]
- b) Find equivalent resistance between AB for the circuit shown in fig. 7.b [07]

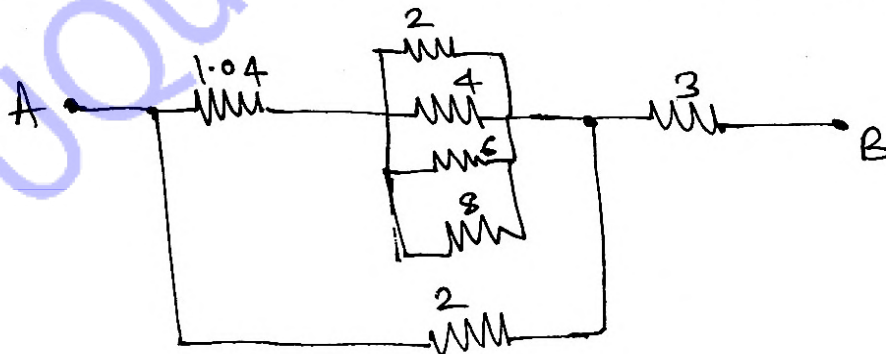


Fig. 7 (b)

OR

- Q.8 a) For the circuit shown in fig. 8.a find the current flowing through PQ [06]
using Kirchhoff's laws.

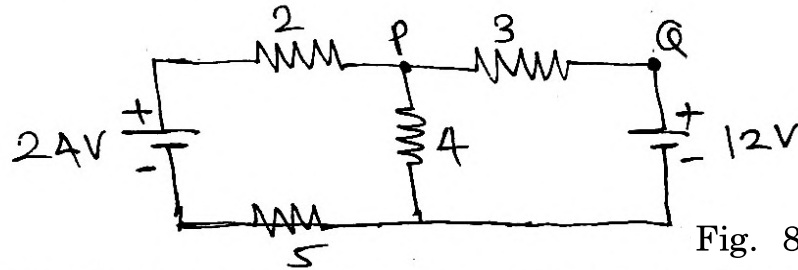


Fig. 8 (a)

- b) Write down the steps to find current through load resistance R_L using Thevenin theorem for the circuit shown in fig. 8.b. [07]



Fig. 8 (b)