

Total No. of Questions : 4]

PC378

SEAT No. :

[Total No. of Pages : 1

[6358]-109

F.E. (Insem)

BASIC ELECTRONICS ENGINEERING
(2019 Pattern) (Semester - I) (104010)

Time : 1 Hour]

[Max. Marks : 30

Instructions to the candidates:

- 1) Answer Q.1 or Q.2, Q.3 or Q.4.
- 2) Assume suitable data if necessary.

Q1) a) Explain forward biasing of P-N Junction diode with its V-I characteristics. [5]

b) Compare half wave, center tapped transformer full wave rectifier and Bridge full wave rectifier. [5]

c) Draw and explain voltage regulator circuit using zener diode. [5]

OR

Q2) a) What is depletion region? Explain the effect of forward biasing and reverse biasing of P-N Junction diode on depletion region. [5]

b) For Bridge full wave rectifier, applied input voltage is $10\sin \omega t$, calculate average output voltage, RMS voltage and PIV rating of diode used. [5]

c) Explain principle of operation and construction of photodiode. List its applications. [5]

Q3) a) Explain BJT as an amplifier in common Emitter configuration. [5]

b) Explain construction and operation of N-channel EMOSFET. [5]

c) For an inverting amplifier using Op-Amp if $R_f = 10k\Omega$, $R_i = 1k\Omega$ and $V_{cc} = \pm 15V$ calculate ' V_o ' for $V_{in} = 100\text{ mv}$. [5]

Comment on the phase relation between input and output voltage.

OR

Q4) a) Explain regions of operation of transistor with respect to biasing conditions. For BJT, if $J_B = 10\text{ }\mu\text{A}$ and $I_E = 1\text{ mA}$ [5]

Calculate value of I_c and β (Beta).

b) Compare BJT and MOSFET. [5]

c) Draw and explain Op-amp as inverting amplifier. Write the expression for voltage gain. [5]

