

Total No. of Questions : 5]

SEAT No. :

P5125

[Total No. of Pages : 2

[5823]-105

F.Y. B.Sc. (Computer science)

ELECTRONIC SCIENCE

ELC - 111 : Semiconductor Devices and Basic Electronic  
Systems (Backlog)

(CBCS) (2019 Pattern) (Semester - I) (Paper - I)

Time : 2 Hours]

[Max. Marks : 35

Instructions to the candidates:

- 1) Q.1 is compulsory.
- 2) Solve any three questions from Q.2 to Q.5.
- 3) Questions 2 to 5 carry equal marks.
- 4) Draw neat labeled diagrams wherever necessary.

Q1) Solve any five of the following :

[5 × 1 = 5]

- a) Draw symbols for :
  - i) LED
  - ii) Zener diode
- b) What is piezoelectric effect?
- c) State types of MOSFET.
- d) Define knee voltage.
- e) "IC 555 astable multivibrator is used as a clock" \_ state true or false.
- f) What is output voltage of IC 7805?

Q2) Answer the following :

- a) Explain construction and working of opto coupler. [4]
- b) Explain working of transistor as a switch. [3]
- c) Draw block diagram of SMPS and explain its operation in brief. [3]

Q3) Answer the following :

- a) Define the terms  $\alpha$ ,  $\beta$  and  $\gamma$  with reference to transistor. State the relationship between  $\alpha$  and  $\beta$ . [4]

P.T.O.

- b) Draw diagram of full wave rectifier using two diodes with filter capacitor. Define ripple factor. [3]
- c) Draw diagram of IC 555 timer. For  $R_A = 8k\Omega$ ,  $R_B = 4k\Omega$  and  $C = 0.1\mu F$ ; calculate the output frequency. [3]

**Q4)** Answer the following :

- a) Explain working of zener diode as a voltage regulator. [4]
- b) State Barkhausen Criteria for sustained oscillations. Find output frequency of wien bridge oscillator [3]  
if  $R_1 = 1k\Omega$ ,  $C = 0.22\mu f$  ;
- c) Draw diagram of 2 bit flash ADC and explain its working. [3]

**Q5)** Attempt any four of the following : [4 × 2.5 = 10]

- a) Explain need of Digital to Analog converter.  
Draw diagram of R-2R ladder network.
- b) Write a short note on crystal oscillator.
- c) Explain how MOSFET works as a switch.
- d) Draw block diagram of successive approximation ADC.
- e) Write a short note on potential divider bias of transistor.
- f) Draw block diagram of off - line UPS.

