Total	No.	of	Ques	tions:	51

SEAT No.:		
[Total	No. of Dogos 21	

[Total No. of Pages: 2]

# F.Y. B.Sc. (Computer Science) **ELECTRONICS SCIENCE**

# ELC 112: Principles of Digital Electronics (Backlog)

(2019 Pattern) (CBCS) (New) (Paper - II) (Semester - I)

[Time: 2 Hours]

[Max. Marks: 35]

Instructions to the candidates:

- 1) Q. 1 is compulsory.
- 2) Solve any three questions from Q.2 to Q.5.
- 3) Questions 2 to 5 carry equal marks.

#### Q.1) Solve any Five of the following:

 $[5 \times 1 = 5]$ 

- a) Define fan out terms.
- b) Draw symbol and truth table of OR logic.
- c) What is Non-weighted code?
- d) How many select lines are required to design 1:4 Demultiplexer?
- e) What is base of hexadecimal number system?
- f) State the function of IC 7447.

### Q.2) A) Attempt the following:

- i) Simplify the following expression using k-map.
- [3]

$$Y = \overline{ABC} + A\overline{BC} + ABC + AB\overline{C}$$

ii) Write a short note on multiplexer.

- [3]
- B) Design Gray to Binary converter using k- map technique.
- [4]

P.T.O.

#### Q.3) A) Attempt the following:

i) Write a short note on karnaugh map technique.

- [3]
- ii) Explain Half adder with neat logic diagram and truth table.
- [3]
- **B)** Draw the logic diagram for the given Boolean expression and write the truth table for it.

[4]

$$Y=(A+\overline{B})+(BD)+(\overline{A}\ \overline{B}\ \overline{C})$$

### Q.4) A) Attempt the following:

i) Perform the following:  $1)(1010)_2 = (?)_{Gray}$ 

[3]

- $2)(101010110)_2 = (?)_{BCD}$
- $(3)(AF)_{16} = (?)_{BCD}$
- ii) Convert the following expression into standard SOP form. [3]

$$Y=AB + A\overline{C} + BC$$

B) Draw and explain the logic diagram of 1:4 demultiplexer and explain it. [4]

### Q.5) Attempt any Four of the following:

 $[4 \times 2\frac{1}{2} = 10]$ 

- a) Write a short note on ASCII.
- b) Design AND, OR and NOT logic using NOR gate.
- c) What is Binary number? Where is it used?
- d) Write a short note on Basic gates.
- e) Explain the concept of parity bits and where it is used?
- f) Write a short note on encoder?





