

[Total No. of Questions: 5]

SEAT No. :

[Total No. of Pages: 2]

F.Y.B.Sc. (Computer science)

ELECTRONIC SCIENCE

**ELC - 111: Semiconductor Devices and Basic Electronic Systems
(Backlog)**

(CBCS) (2019 Pattern) (Semester - I) (Paper - I)

[Time: 2 Hours]

[Max. Marks: 35]

Instructions to the candidates:

- 1) *Q.1 is compulsory.*
- 2) *Solve any three questions from Q.2 to Q.5.3)*
Questions 2 to 5 carry equal marks.
- 4) *Draw neat labeled diagrams wherever necessary.*

Q1) Solve any five of the following:

[5 × 1 = 5]

- a) Draw symbols for :
 - i) LED.
 - ii) Zener diode.
- b) What is full form of MOSFET?
- c) What is ripple in rectifier?
- d) State two conditions of Barkhausen criteria.
- e) State the name of fastest ADC.
- f) "MOSFET is unipolar device" state true or false.

Q.2) A) Attempt the following:

i) Compare half and full wave rectifier. **[3]**

ii) Explain working principle of astable multivibrator. **[3]**

B) Explain construction and working principle of LED. **[4]**

Q.3) A) Attempt the following:

- i) With neat diagram explain working of in n-channel the DEMOSFET. [3]
- ii) Compare CB, CE and CC configuration of transistor (any three). [3]

B) Calculate the analog output for 4 bit R-2R ladder DAC for input assume logic 0= 0V, logic 1= 1V.

- (i) 1001 (ii) 0001 (iii) 1010 (iv) 1000 [4]

Q.4) A) Attempt the following:

i) Define the following terms with respect to power supply:

- (1) Ripple factor (2) Peak inverse voltage (3) Load regulation. [3]

ii) An astable 555 multivibrator has $R_A=9.6 \text{ k}\Omega$, $R_B=7.2 \text{ k}\Omega$ and

$C = 0.01 \mu\text{f}$ what is the output frequency. [3]

B) Explain working of N-P-N transistor in detail. [4]

Q.5) Attempt any four of the following:

[4 × 2.5 = 10]

- a) Write a short note on solar cell.
- b) Explain working of BJT as a switch.
- c) Draw the diagram of drain characteristics of n-channel EMOSFET.
- d) Write a short note on Zener diode as a voltage regulator.
- e) In wein bridge oscillator $R = 2 \text{ k}\Omega$, $C = 0.51 \mu\text{f}$ calculate the frequency of oscillator.
- f) State the application of ADC.

