

Total No. of Questions : 5]

SEAT No. :

PA-1006

[Total No. of Pages : 3

[5902]-25

F.Y. B.Sc. (Computer Science)

ELECTRONICS

ELC - 121 : Instrumentation System

(New 2019 Pattern) (Semester - II) (CBCS) (Paper - I)

Time : 2 Hours ]

[Max. Marks : 35


Instructions to the candidates:

- 1) Question 1 is compulsory.
- 2) Solve any three questions from Q.2 to Q.5.
- 3) Figures to the right indicate full marks.
- 4) Draw neat diagrams wherever necessary.
- 5) Questions 2 to 5 carry equal marks.

Q1) Solve any five of the following.

[5×1=5]

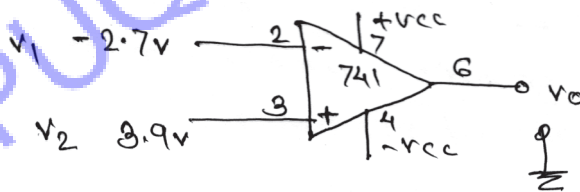- a) What is full form of CCD?
- b) What is sensor? Give any one example.
- c) Define dark Resistance w.r.t to LDR.
- d) What is input offset voltage?
- e) What is thick flim sensor?
- f) Find the output of the following circuit.



Q2) a) Attempt any two of the following:

[2×3=6]

- i) Write short note on Tilt Sensor.
  - ii) With the help of neat diagram, explain working principle of stepper motor.
  - iii) What is Flim sensor? Which are two types of flim sensor? Give any two application of flim sensors.
- b) Draw the circuit diagram of op.Amp as subtractor and drive the expression for its output voltage.

[1×4=4]



P.T.O.

- Q3) a)** Attempt any two of the following: **[2×3=6]**
- i) State working principle of ultrasonic sensor. State any two application of ultrasonic sensor.
  - ii) Draw smart instrumentation system. Give two advantages.
  - iii) What is thermistors? Give the equation of resistance change with respective to temperature for thermistor.
- b) Draw the circuit diagram of op-Amp as adder and drive the expression for its output voltage. **[1×4=4]**

- Q4) a)** Attempt any two of the following: **[2×3=6]**
- i) Draw the block diagram of an Op-Amp and explain.
  - ii) Write a short note on PIR sensor.
  - iii) In Non inverting amplifier  $v_{in} = 6.5v$  where  $R_F = 24k$ ,  $R = 4k\Omega$  find the value of
    - 1) Output voltage
    - 2) Voltage gain
- b) Explain LDR on the basis of the following points:- Working principle, structure and symbol, material used, its application. **[1×4=4]**

- Q5) Attempt any Four of the following:** **[4×2.5=10]**
- a) What is transducer? Define following with respective to sensor.
    - i) Accuracy
    - ii) Sensitivity
  - b) Explain working principle of DC motor.
  - c) Write a short note on LM-35.
  - d) What is nanosensors? How nanosensors are fabricated? Give any limitation of nanosensors.
  - e) Explain the concept of virtual ground in Op-Amp.

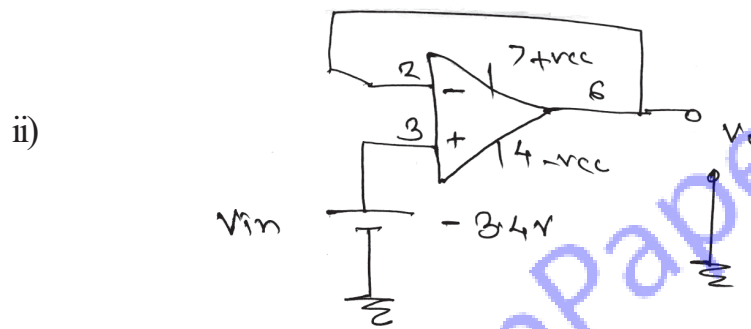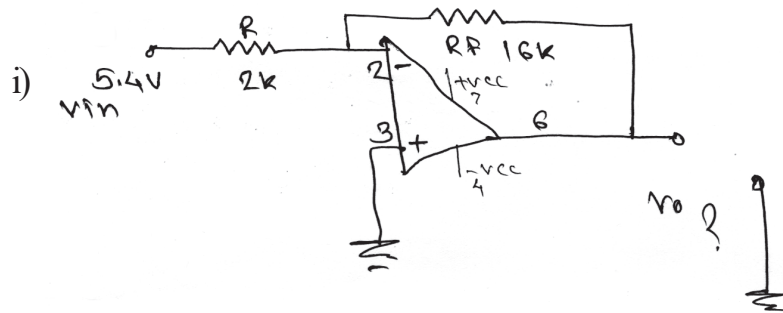- f) Identify the following Op-Amp configurations and find their output voltages.



www.rss