

[Total No. of Questions: 5]

SEAT No. :

[Total No. of Pages: 2]

F.Y.B.Sc. (Computer Science)
ELECTRONIC SCIENCE
ELC-122: Basics of Computer Organization (Backlog)
(New 2019 Pattern) (CBCS) (Semester -II) (Paper-II)

[Time: 2 Hours]

[Max. Marks: 35]

Instructions to the candidates:

- 1) *Question 1 is compulsory.*
- 2) *Solve any three questions from Q.2 to Q.5.*
- 3) *Figures to the right indicate full marks.*
- 4) *Draw neat diagrams wherever necessary.*
- 5) *Questions 2 to 5 carry equal marks.*

Q.1) Solve any five of following.

[5]

- a) Draw the logic symbol of SR flip flop.
- b) Write full form of T flip-flop.
- c) Define Counter.
- d) What is virtual memory?
- e) State any two applications of shift registers?
- f) Using 10 address lines _____ word can be addressed.

Q.2) A) Attempt the following:

i) Draw logic diagram of 3 bit SISO shift register in right shift mode and explain its working.

[3]

ii) Explain basic computer organization with block diagram.

[3]

B) Draw neat block diagram of CPU and explain working of each block.

[4]

Q.3) A) Attempt the following:

i) What is ring counter? Draw and explain it. [3]

ii) Discuss various types of memories used in computer in short. [3]

B) Explain the concept of J-K flip flop and draw its block diagram with truth table. [4]

Q.4) A) Attempt the following:

i) Explain concept of T flip flop in detail. [3]

ii) What is important of I/O interface discuss details. [3]

B) Explain in brief need of cache memory. [4]

Q.5) Attempt any Four of the following:

[4 × 2.5 = 10]

- a) Explain how SR-flip flop can be converted into D-flip flop.
- b) Compare computer architecture and organization.
- c) Draw logic circuit diagram of three bits asynchronous up counter.
- d) Compare CD and DVD (any three).
- e) Write short note on Latch.
- f) How much time required paralleling in and serial out shift a 4 bit data in shift register operation at the clock frequency is 10 KHz.

